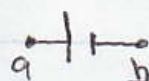





when circuit is open,  $I=0$ , so  $V_{ab} = \mathcal{E}$



good battery:  $r$  small

bad battery:  $r$  big

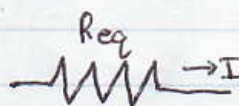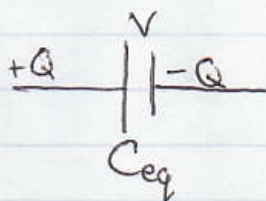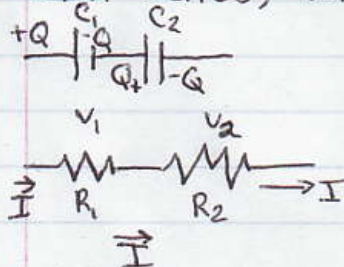In series, voltage add, and the charge & currents are equal.








$$\frac{1}{C_{eq}} = \frac{V}{Q} = \frac{V_1}{Q} + \frac{V_2}{Q} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{R_{eq}} = \frac{I}{V} = \frac{I_1}{V} + \frac{I_2}{V} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \frac{V}{I} = \frac{V_1}{I} + \frac{V_2}{I} = R_1 + R_2$$

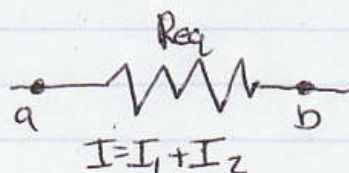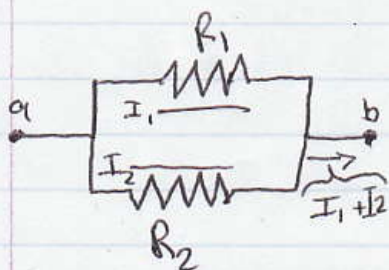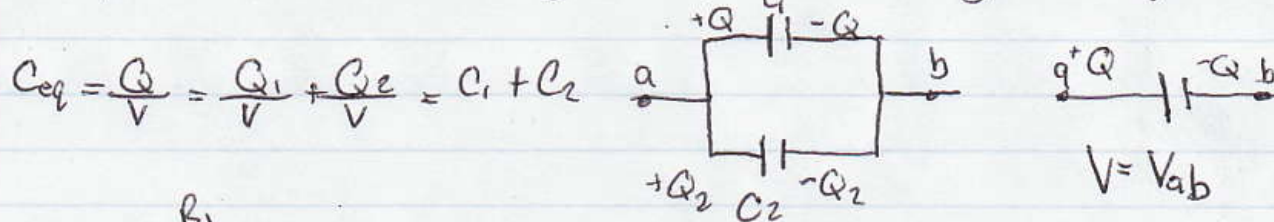In parallel, currents & charges add, and the Voltage are equal




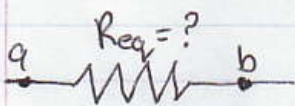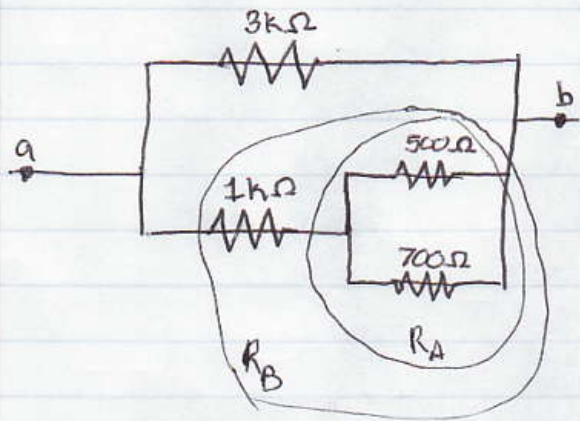

$$\textcircled{1} \frac{1}{R_A} = \frac{1}{500\Omega} + \frac{1}{700\Omega}$$


$$\textcircled{2} R_B = 1k\Omega + R_A$$
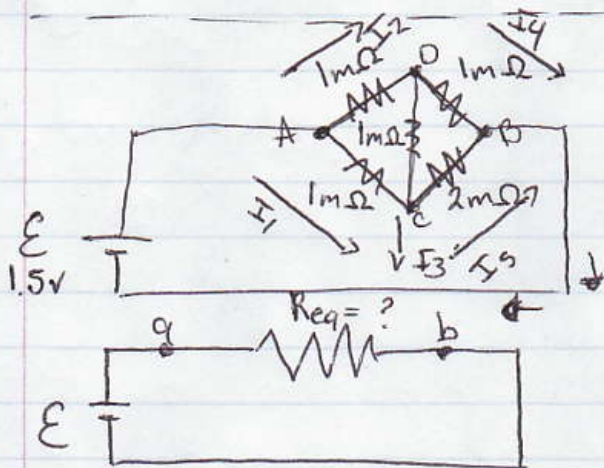
$$\textcircled{3} \frac{1}{R_{eq}} = \frac{1}{3k\Omega} + \frac{1}{R_B}$$



Use Kirchhoff's Rules:


Junction:  
(wire)

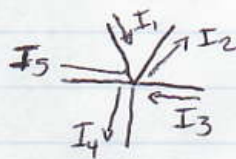

$$I_1 + I_3 = I_2 + I_4 + I_5$$

total incoming current equals total outgoing current

Loop:  
The voltage add to 0 (zero)

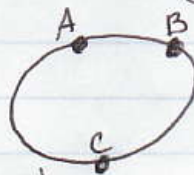

$$V_{ab} + V_{bc} + V_{ca} = 0$$

$$(V_a - V_b) + (V_b - V_c) + (V_c - V_a) = 0$$

Junction:

one more loop:

$$(a) I = I_1 + I_2$$

$$(b) I_4 + I_5 = I$$

$$(c) I_1 + I_3 = I_5$$

$$(d) I_2 = I_3 + I_4$$

$$(adc) 0 = (1\text{m}\Omega)I_2 + (1\text{m}\Omega)I_3 + (1\text{m}\Omega)(-I_1)$$

$$(bcd) 0 = (2\text{m}\Omega)(-I_5) + (1\text{m}\Omega)(-I_3) + (1\text{m}\Omega)I_4$$

$$(acb) 0 = \underbrace{(1\text{m}\Omega)I_1}_{V_{ac}} + \underbrace{(2\text{m}\Omega)I_5}_{V_{cb}} + \underbrace{(-1.5\text{V})}_{V_{bc}}$$

Equivalently:  $V_{ab} = V_{ac} + V_{cb}$

$$V_a - V_b$$

$$\int_b^a -\vec{E} \cdot d\vec{l}$$

7 Equations, 6 variables

$$R_{eq} = \frac{V}{I} = \frac{\mathcal{E}}{I} = \frac{1.5\text{V}}{I} = \frac{5}{6} \text{m}\Omega$$

$$I = 1.8\text{kA}$$

$$I_2 = \frac{11}{24} \cdot 1.8\text{kA}$$

$$I_1 = \frac{13}{24} \cdot 1.8\text{kA}$$

$$I_5 = \frac{15}{24} \cdot 1.8\text{kA}$$

$$I_3 = \frac{1}{12} \cdot 1.8\text{kA}$$

$$I_4 = \frac{3}{8} \cdot 1.8\text{kA}$$

I Divide all the equations by I & used variables


$$x_1 = \frac{I_1}{I} \quad x_2 = \frac{I_2}{I} \quad \dots \quad x_5 = \frac{I_5}{I}$$

and then found

$$R_{eq} = (1\text{m}\Omega)x_1 + (2\text{m}\Omega)x_5 \quad \text{I found } I_3 \text{ last.}$$


$$I = \frac{\mathcal{E}}{R_{eq}}, \quad I_1 = Ix_1, \quad I_5 = Ix_5$$

# Discharging RC circuit

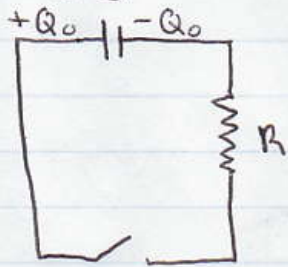

An aside  $P = \frac{V^2}{R}$
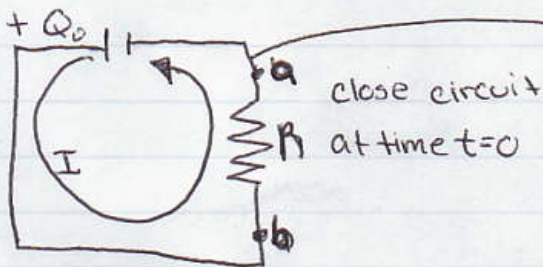
$$\textcircled{5} \frac{dQ}{dt} = \frac{-Q}{RC} \Rightarrow \int_{Q_0}^Q \frac{dQ}{Q} = \int_0^t \frac{-dt}{RC}$$



$$\frac{dQ}{dt} = \underbrace{-I}_{\text{express in terms of } Q \text{ and constant}} = \frac{V}{RC}$$

$C = \frac{Q}{V}$   
 $V = \frac{Q}{C}$   
 $R = \frac{V}{I}$   
 $I = \frac{V}{R}$

~~$V = \frac{Q}{C}$~~


V & I are not constant

$\textcircled{3} \frac{Q/C}{R}$   
 $\frac{Q}{RC}$

$V = V_{ba} = V_D - V_{cr}$

$$\ln\left(\frac{Q}{Q_0}\right) = \frac{-t}{RC}$$

$$Q = Q_0 e^{-t/(RC)}$$

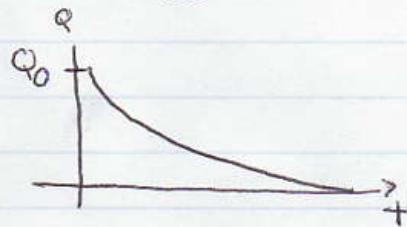

$$I = \frac{-dQ}{dt} = \frac{Q_0}{RC} e^{-t/(RC)}$$

$$V = IR = \underbrace{Q_0}_{V_0} e^{-t/(RC)}$$