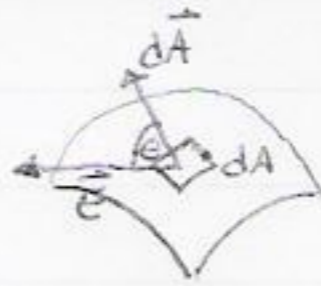


10/11/10


Notes

$$\Phi_E = \int_{\text{surface}} \vec{E} \cdot d\vec{A} = \int E(dA) \cos \theta$$



Gauss' Law $\frac{Q_{\text{enclosed}}}{\epsilon_0} = \Phi_E$ for closed surfaces

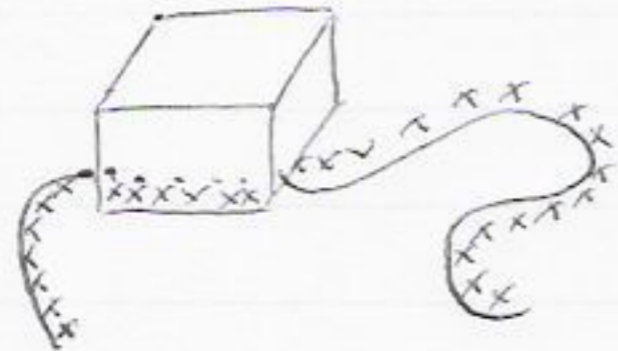Given: $\Phi_E = 4.5 \cdot 10^4 \text{ V}\cdot\text{m}$



$L_{\text{total}} = 3.0 \text{ m}$

$$\frac{dQ}{dL} = \underbrace{2.7 \cdot 10^{-6} \frac{\text{C}}{\text{m}}}_{\text{constant}}$$

Find $\frac{L_{\text{enclosed}}}{L_{\text{total}}}$, same as

$$\frac{Q_{\text{enclosed}}}{Q_{\text{total}}}$$

$$\frac{Q_{\text{enclosed}}}{Q_{\text{total}}} = \frac{(dQ/dL)L_{\text{enclosed}}}{(dQ/dL)L_{\text{total}}}$$

$$\frac{L_{\text{enclosed}}}{L_{\text{total}}}$$

$$\frac{Q_{\text{enclosed}}}{8.1 \cdot 10^{-6} \text{ C}}$$

$$\frac{L_{\text{enclosed}}}{8.1 \cdot 10^{-6} \text{ C}}$$

$$Q_{\text{encl}} = \epsilon_0 \Phi_E \left[8.854 \cdot 10^{-12} \frac{\text{C}^2}{\text{N}\cdot\text{m}^2} \right] = 4.5 \cdot 10^4 \frac{\text{N}\cdot\text{m}}{\text{C}}$$

$$= 3.984 \dots \cdot 10^{-7} \frac{\text{C}^2}{\text{N}\cdot\text{m}^2} \cdot \frac{\text{N}\cdot\text{m}^2}{\text{C}}$$

$$= 3.984 \dots \cdot 10^{-7} \text{ C}$$

$$\frac{L_{\text{encl}}}{L_{\text{total}}} = \frac{Q_{\text{encl}}}{Q_{\text{total}}} = 4.9 \cdot 10^{-2} = 4.9\%$$

$$V_{ab} = - \int_b^a \vec{E} \cdot d\vec{l} \quad \vec{E} = \frac{\vec{F}}{q}$$

1 volt = $\frac{\text{N}}{\text{C}} \cdot \text{m}$



$$Q_{\text{total}} = \int_{\text{string}} dQ = \int_{\text{string}} \frac{dQ}{dL} dL = \frac{dQ}{dL} \int_{\text{string}} dL = \frac{dQ}{dL} \cdot L_{\text{total}}$$



$$2.7 \cdot 10^{-6} \text{ C/m} = 2.7 \mu\text{C/m}$$

A $Q = Q_0 e^{-t/\tau}$ ← Discharging RC circuit

$\tau = RC$

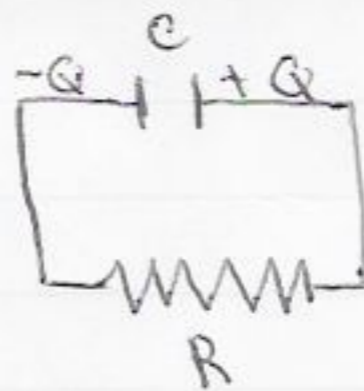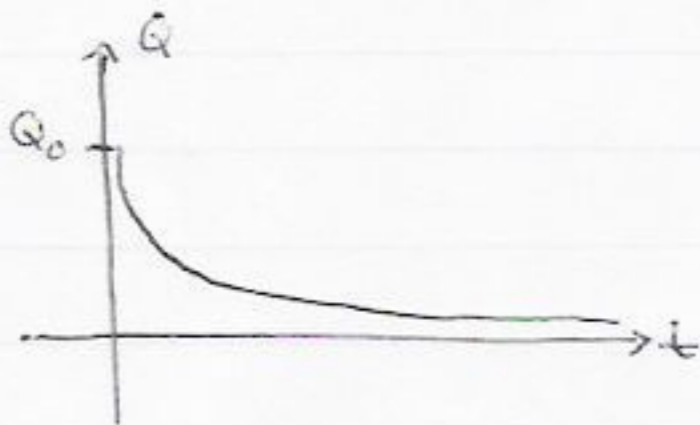

Solve $Q = \frac{1}{2} Q_0$ for $t \longrightarrow \frac{1}{2} Q_0 = Q_0 e^{-t/\tau}$

Given $\tau = 1.32 \cdot 10^{-5} \text{ s}$

$\ln \frac{1}{2} = -t/\tau$

$-\tau \ln \frac{1}{2} = t$

$-0.093147 \dots$

$9.1495 \dots \cdot 10^{-6} \text{ s} = t$

$9.15 \cdot 10^{-6} \text{ s} = t$

MT #5b

$U = \frac{1}{2} U_0$ for t

$\frac{Q^2}{2C} = U$

$\frac{Q^2}{2C} = U = \frac{1}{2} U_0 = \frac{Q_0^2}{4C}$

$V_{ab} = - \int_b^a \vec{E} \cdot d\vec{l} = - \int_b^a \frac{\vec{F}}{q} \cdot d\vec{l} = \frac{1}{q} \left(- \int_b^a \vec{F} \cdot d\vec{l} \right)$

$U_{ab} = -W_{ab} = - \int_b^a \vec{F} \cdot d\vec{l}$


U_{ab}

$V = \frac{U}{q}$

To charge a capacitor, you go from $q=0$ to $q=Q$

$U = \int_{b=0}^{a=Q} \frac{V dq}{dU} = \int_{a=0}^{a=Q} \frac{q}{C} dq = \frac{1}{C} \int_0^Q q dq = \frac{1}{C} \cdot \frac{1}{2} Q^2$

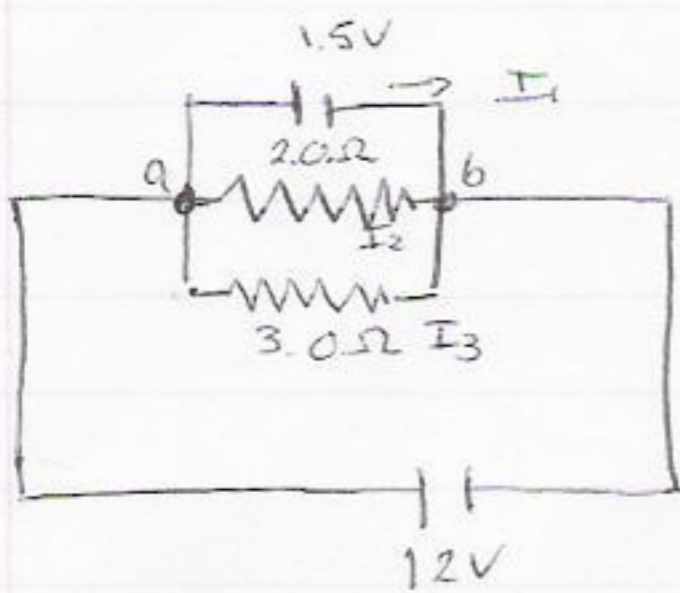$\frac{Q_0^2}{2} = Q^2 \rightarrow \frac{Q_0}{\sqrt{2}} = Q = Q_0 e^{-t/\tau} \rightarrow \frac{1}{\sqrt{2}} = e^{-t/\tau} \rightarrow \ln \frac{1}{\sqrt{2}} = \frac{-t}{\tau} = -t \ln \frac{1}{\sqrt{2}} \Rightarrow t = 4.57 \cdot 10^{-6}$



↑
Lie!!!


What is power being lost to heat through the 3.0Ω resistor?

$$P = I^2 R = \frac{V^2}{R}$$


$$P = I_3^2 (3.0\Omega) = \frac{V_{ab}^2}{3.0\Omega} = \frac{(12V)^2}{3.0\Omega} = \frac{144}{3} W = 48W$$

$$I_3 = \frac{V_{ab}}{3.0\Omega} = \frac{12V}{3.0\Omega} = 4A \rightarrow P = 4^2 \cdot 3 W = 48W$$

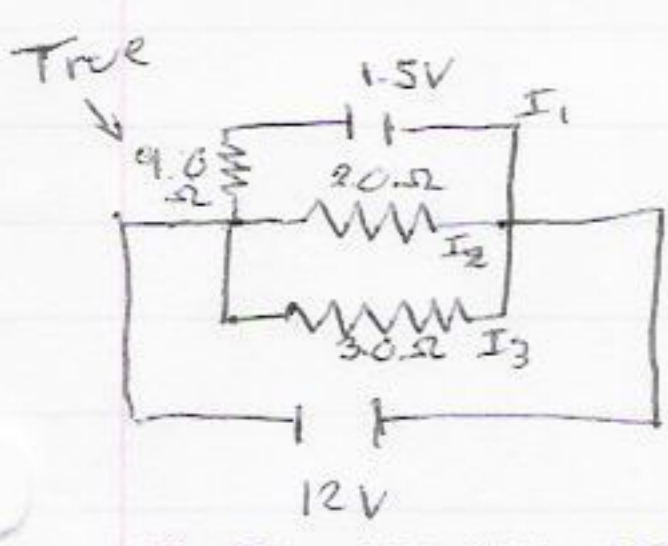In parallel, Voltage equal; current & charges add
In series, current & charges equal; voltages add.



What is the charge on the capacitor?

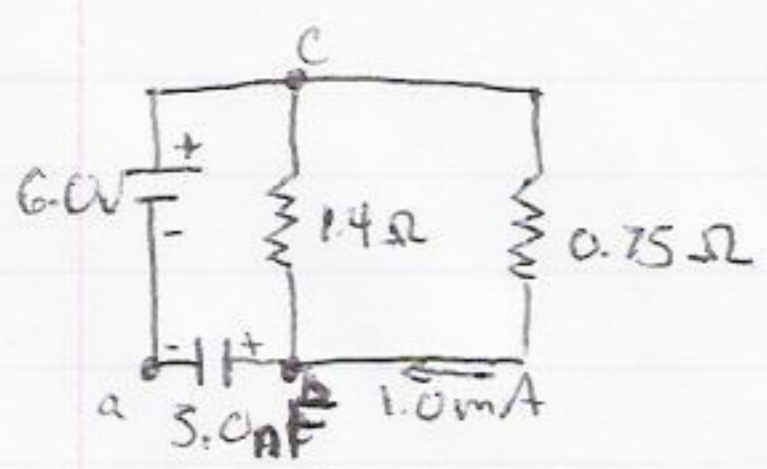

$$V_{cb} = I_1 (1.4\Omega) = (1.0mA) 0.75\Omega = 0.75 \text{ mV} = 7.5 \cdot 10^{-4} V$$

$$V_{ca} + V_{ab} = 6.0V + V_{ab}$$

$$V_{ab} = 7.5 \cdot 10^{-4} V - 6.0V = -5.9925V$$

$$V_b - V_a = V_{ba} =$$

$$C = \frac{Q}{V_{ba}}$$

$$Q = C V_{ba} = 5.0 \times 10^{-9} F \cdot 5.9925V = 3.0 \times 10^{-9} C$$

$\frac{coulomb}{volt}$