

$$\mathcal{E}_2 = -N_2 d\Phi_{B2}/dt$$

Magnetic Flux inside coil caused by current I_1 from coil 1. Because $\mathcal{E}_2 \propto I_1$

More about inductance (two coils)

mutual inductance $M = \frac{-\mathcal{E}_1}{dI_2/dt} = \frac{-\mathcal{E}_2}{dI_1/dt} = \frac{+N_1 d\Phi_{B2}/dt}{dI_1/dt} = \frac{+N_1 \Phi_{B2}}{I_1}$

Last time,


self inductance one coil

$$L = \frac{-\mathcal{E}}{dI/dt} = \frac{+N d\Phi_B/dt}{dI/dt} = \frac{N \Phi_B}{I}$$


often easier to compute

Because $\Phi_B \propto I$

coaxial cable

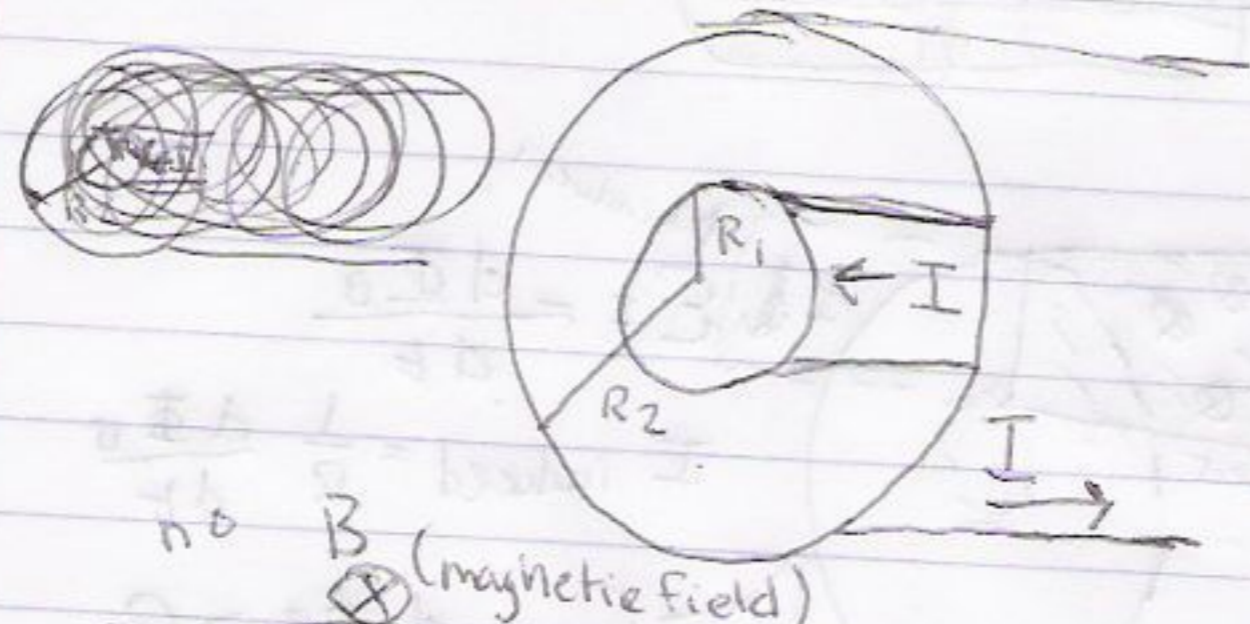

$$L = \frac{1 \cdot \Phi_B}{I}$$

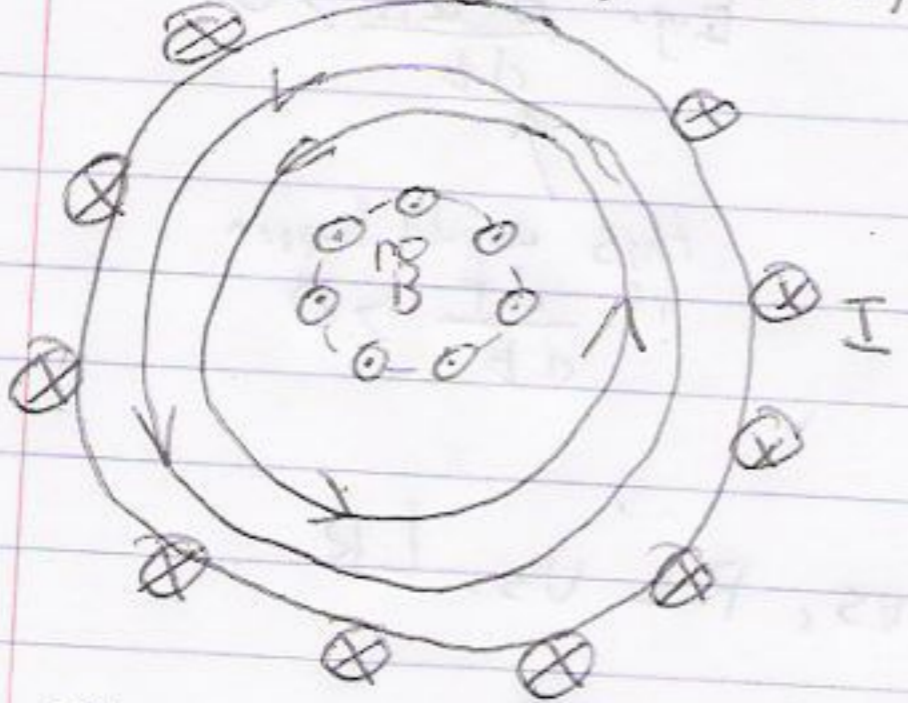


$I =$ total current on each ring


By symmetry
 $B \cdot 2\pi r = \mu_0 I$
 $\Rightarrow B = \mu_0 I / (2\pi r)$
 $\Rightarrow B = 0$
 $B \cdot 2\pi r_i = \mu_0 \cdot 0$
 $B \cdot 2\pi r_o = \mu_0 \cdot 0$
 $\Rightarrow B = 0$

Ampere Law
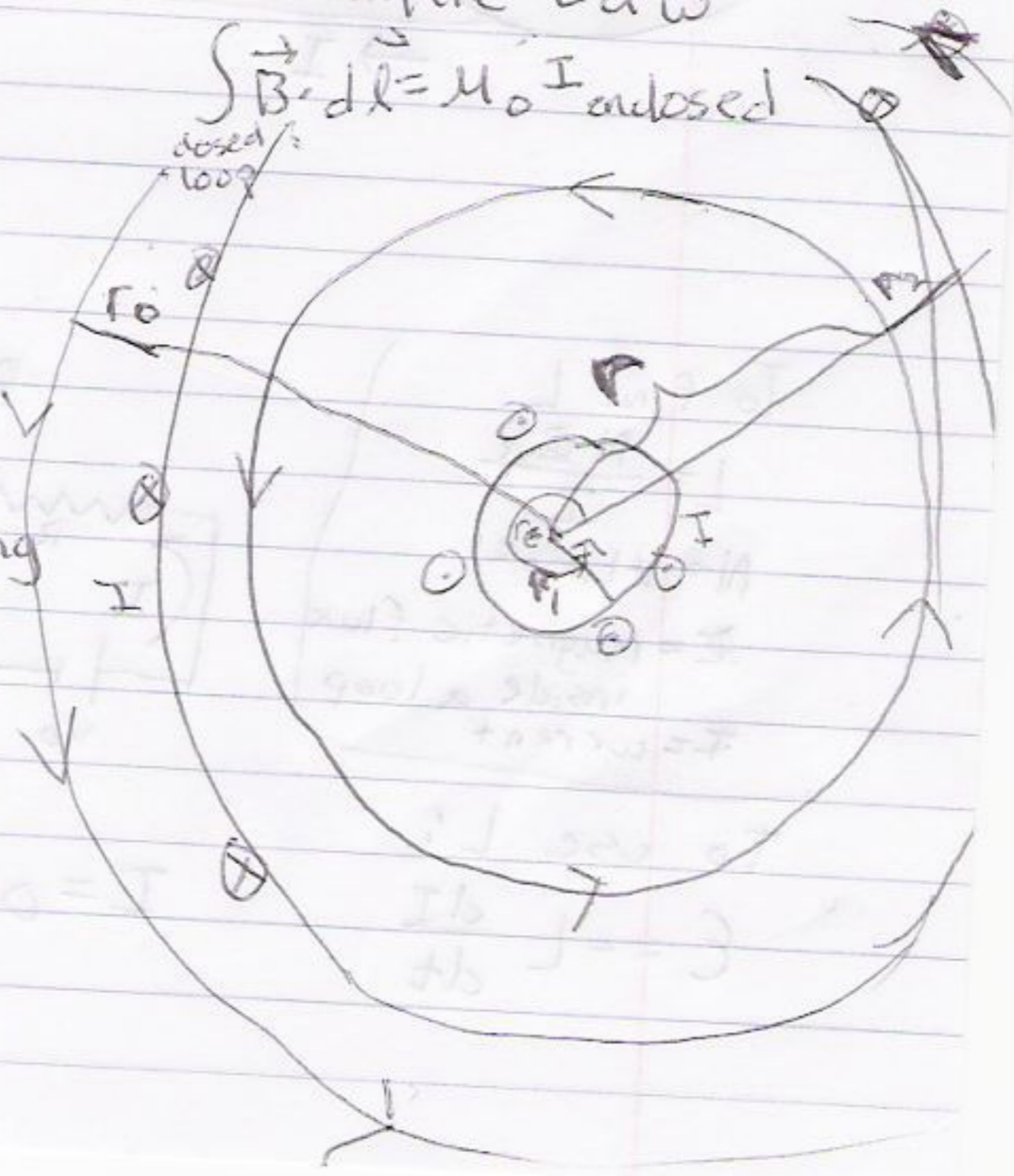
$$\oint \vec{B} \cdot d\vec{l} = \mu_0 I_{\text{enclosed}}$$



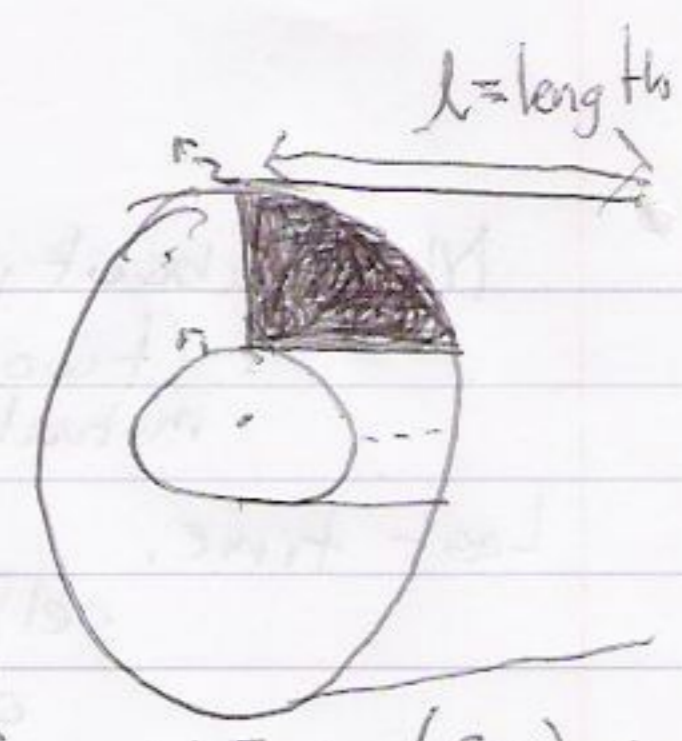Inductance of a solenoid
 Consider a solenoid of length \$l\$ and cross-sectional area \$A\$.




$$L = \frac{1}{I} \cdot \Phi_B \quad \Phi_B = \int_{\text{area}} \vec{B} \cdot d\vec{A}$$

$$\int_{\text{length}} \int_{r_1}^{r_2} \frac{\mu_0 I}{2\pi r} dr dl = \frac{\mu_0 I}{2\pi} \ln\left(\frac{r_2}{r_1}\right) l$$

$$L = \frac{1}{I} \cdot \Phi_B = \frac{\mu_0 I \ln\left(\frac{r_2}{r_1}\right) l}{2\pi I}$$
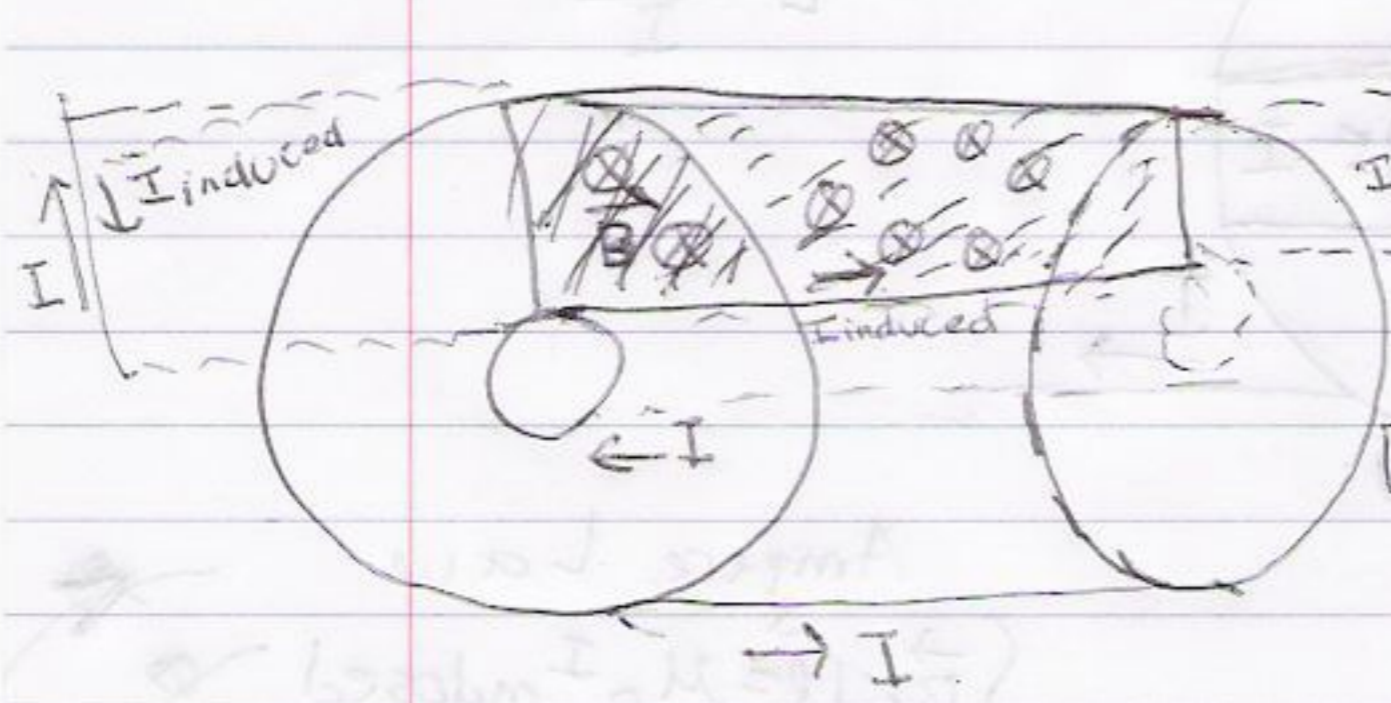
$$= \frac{\mu_0 \ln\left(\frac{r_2}{r_1}\right) l}{2\pi}$$




$$\mathcal{E} = - \frac{d\Phi_B}{dt}$$

$$I_{\text{induced}} = \frac{1}{R} \frac{d\Phi_B}{dt}$$

E.g. $\frac{d\Phi_B}{dt} > 0$
 This would happen if $\frac{dI}{dt} > 0$




To find L
 $L = \frac{N \Phi_B}{I}$
 $N = \# \text{Loops}$
 $\Phi = \text{magnetic flux inside a loop}$
 $I = \text{current}$

R vs. RC vs. LR

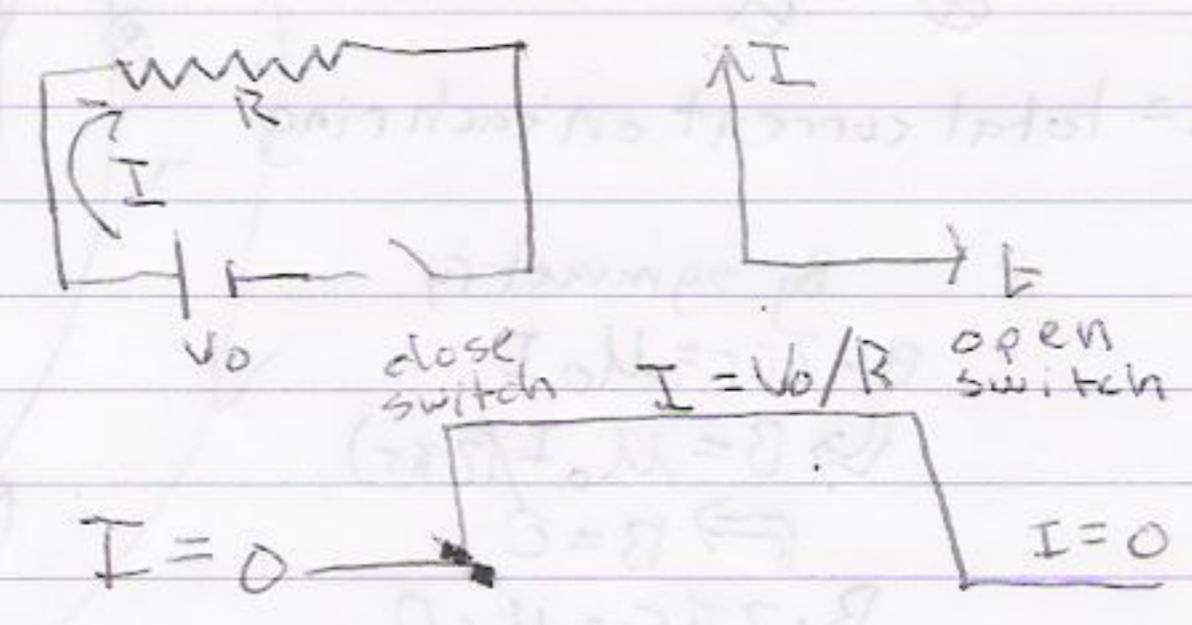


To use L:
 $\mathcal{E} = -L \frac{dI}{dt}$

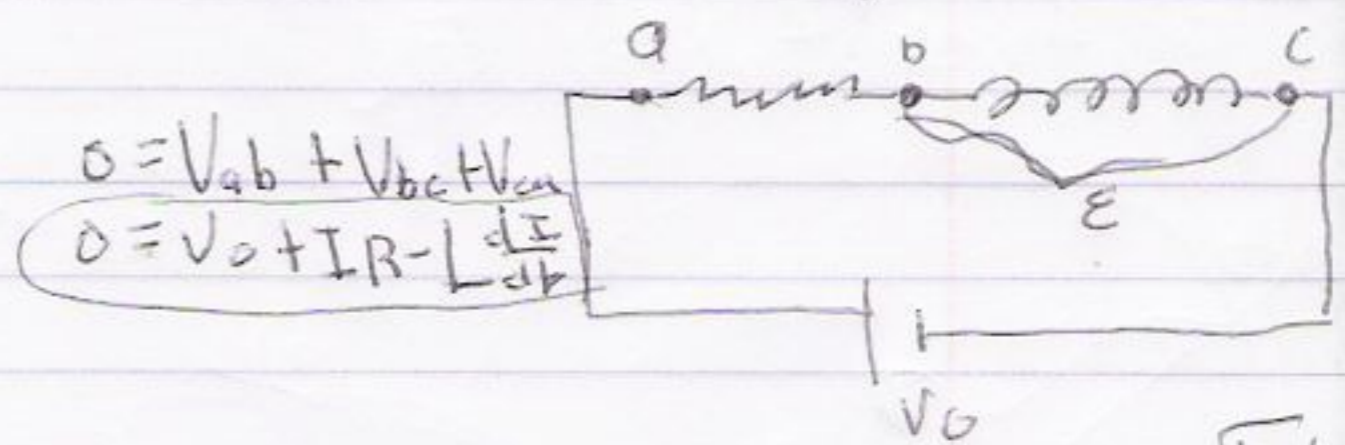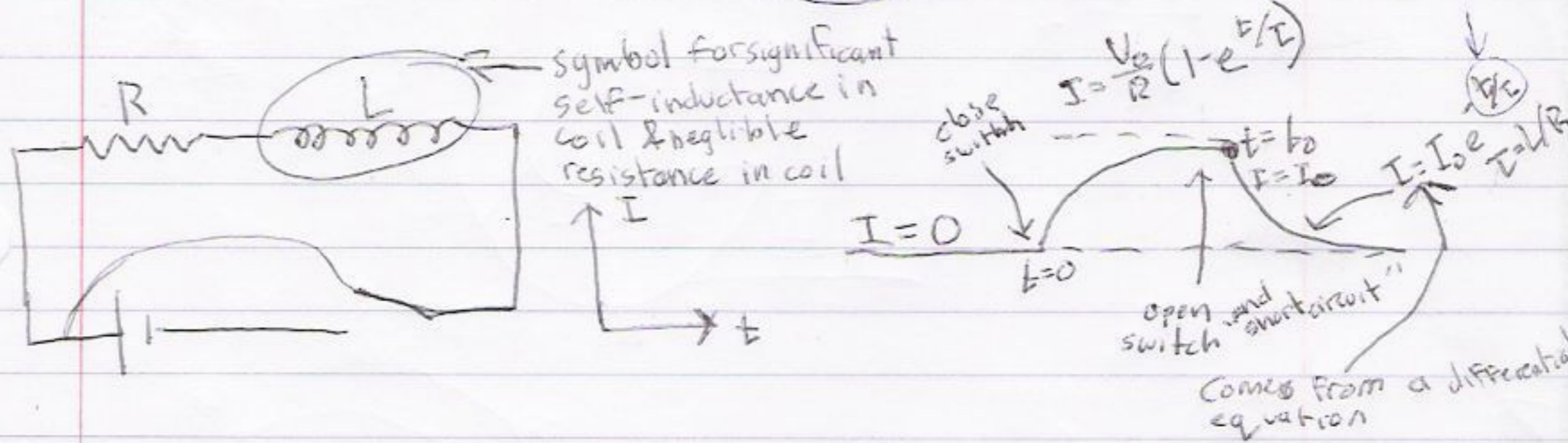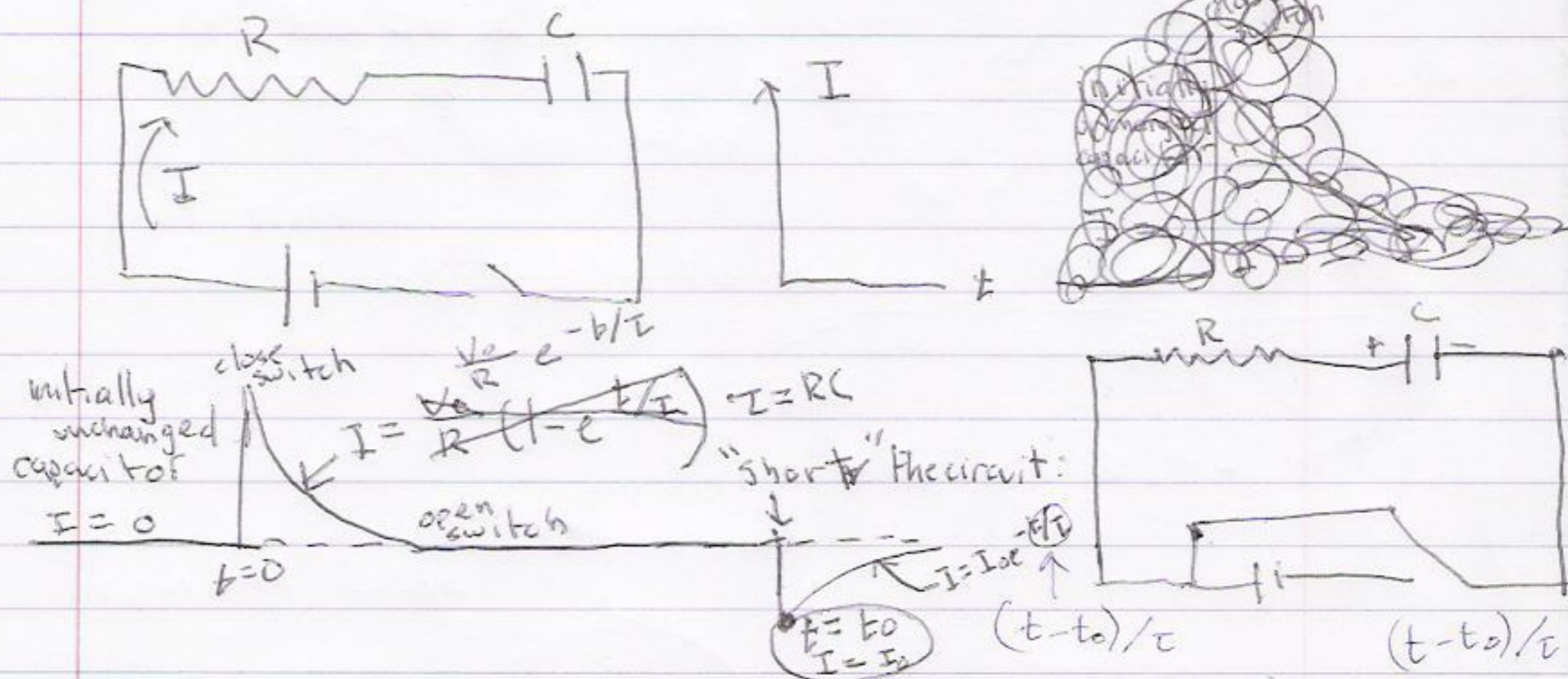$I = 0$ (when switch is closed) $I = 0$ (when switch is open)









LC circuit

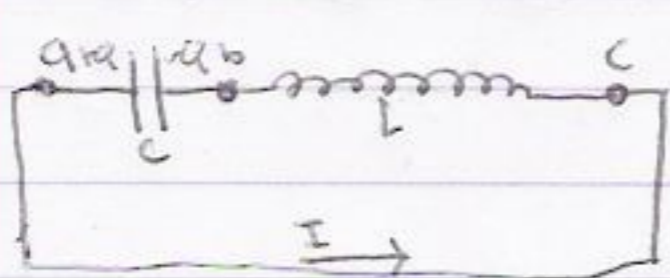

$0 = V_{ab} + V_{bc} + V_{ca}$
 $0 = \frac{Q}{C} - L \frac{dI}{dt} + 0$
 because $C = \frac{Q}{V_{ab}}$
 $0 = \frac{Q}{C} + L \frac{d^2Q}{dt^2}$
 $0 = \frac{d^2Q}{dt^2} + \frac{1}{LC} Q$

Undamped spring:

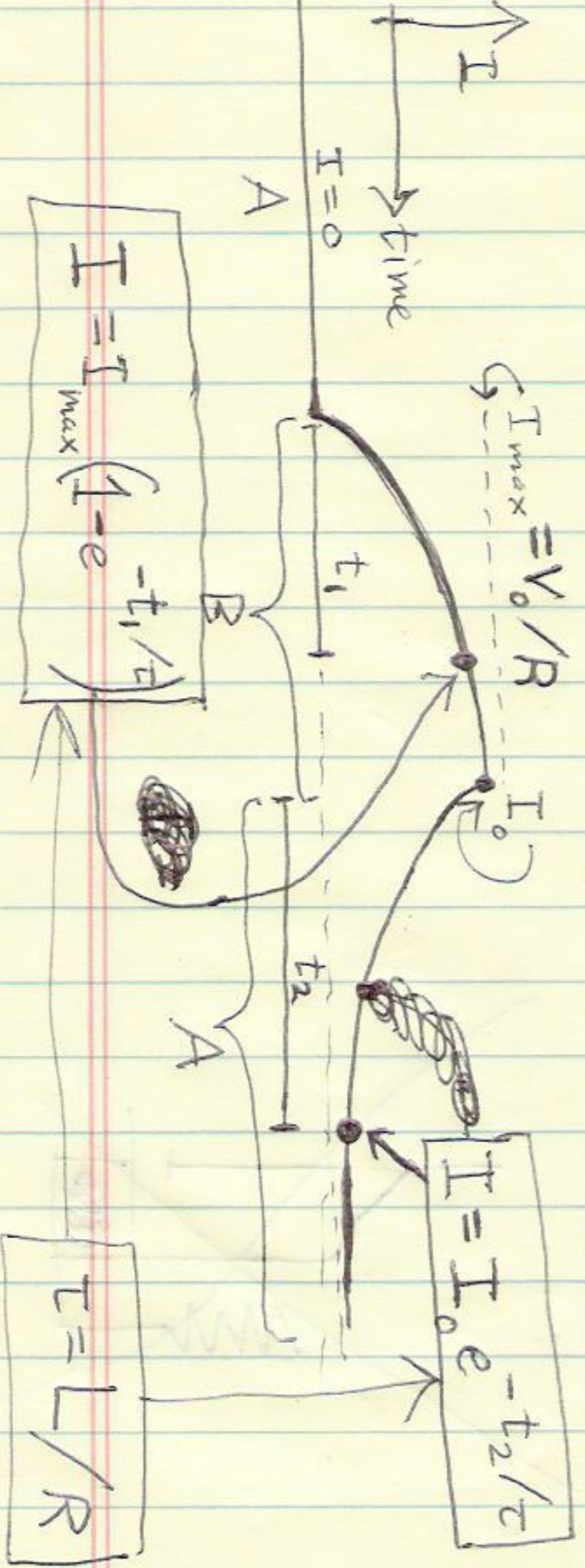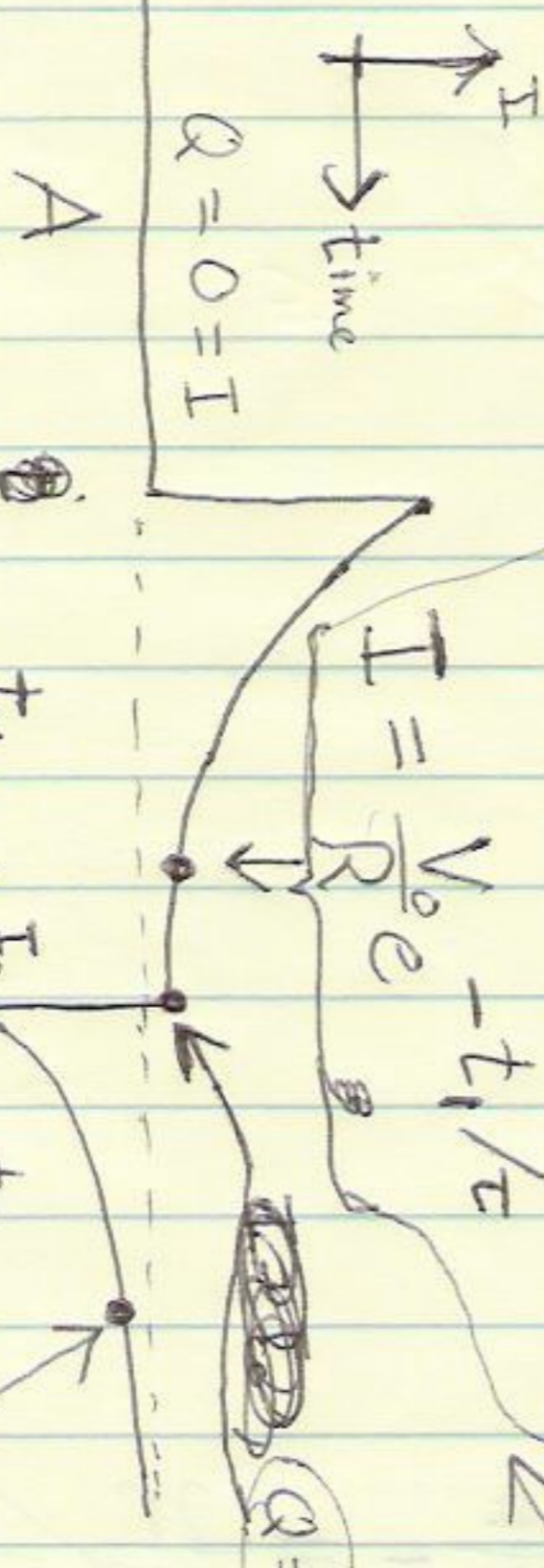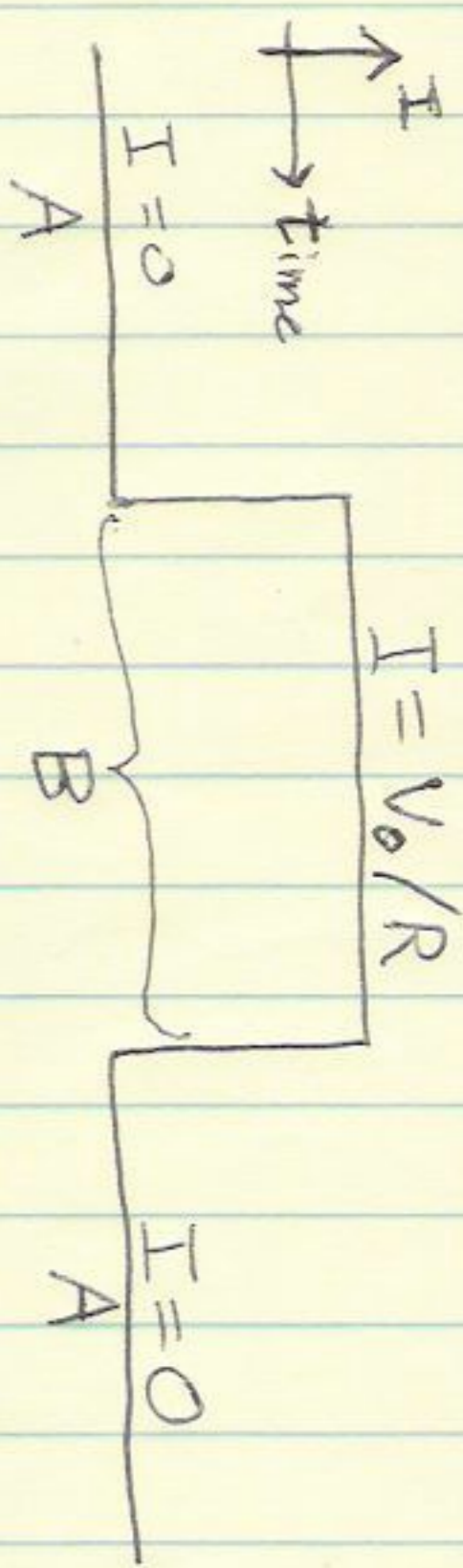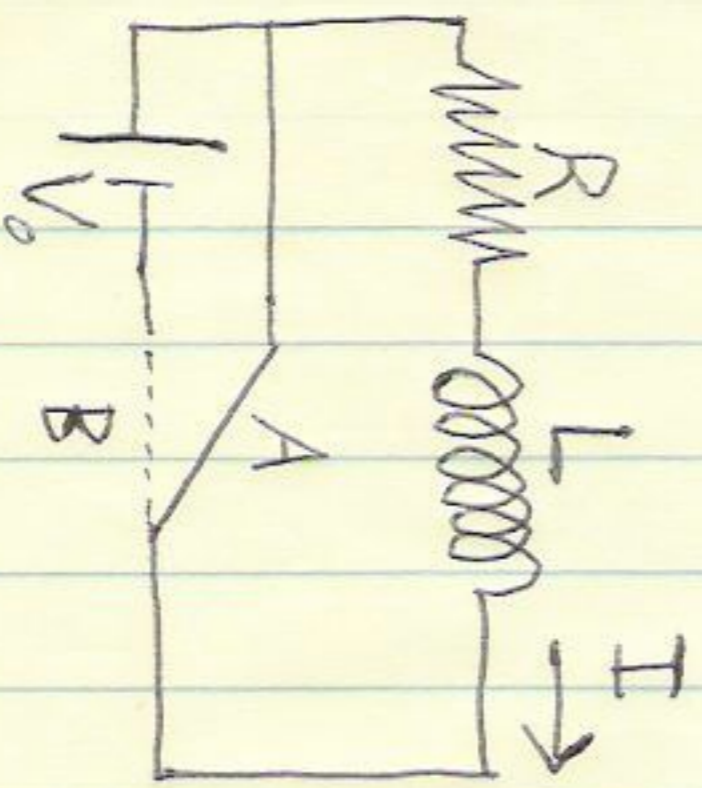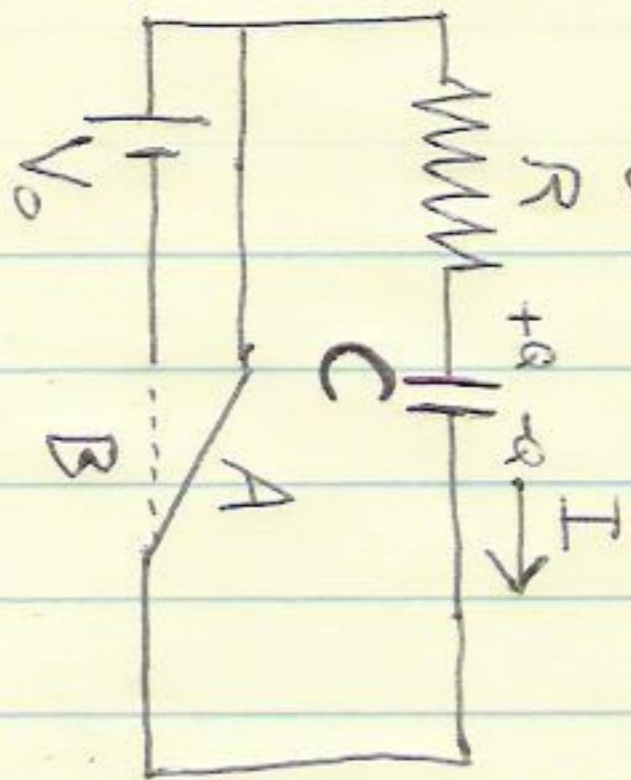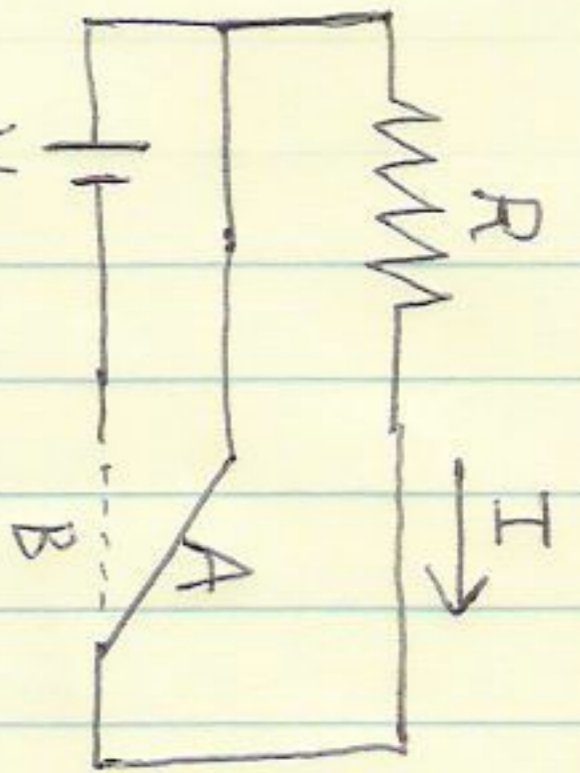$0 = \frac{d^2x}{dt^2} + \frac{k}{m} x$
 solution: $x(t) = A \sin(\omega t + \phi)$
 $\omega = \sqrt{\frac{k}{m}}$
 $\omega = \frac{1}{\sqrt{LC}}$
 $T = \frac{2\pi}{\omega} = 2\pi \sqrt{LC}$
 constant from initial conditions
 $A = \text{max}$



$I = I_{\max} (1 - e^{-t/\tau})$ vs. RC vs. LR circuits
 $I = I_0 e^{-t/\tau}$ vs. LR circuits
 $\tau = RC$
 $\tau = L/R$