

$$C = \epsilon \frac{A}{d}$$

ϵ = permittivity of material inside gap


$$\epsilon = k \epsilon_0$$

dielectric constant

$$V_{ac} = V_a - V_c = \int_c^a -\vec{E} \cdot \vec{dl} = 0$$

$\vec{E} = \vec{0}$ inside conductive wire
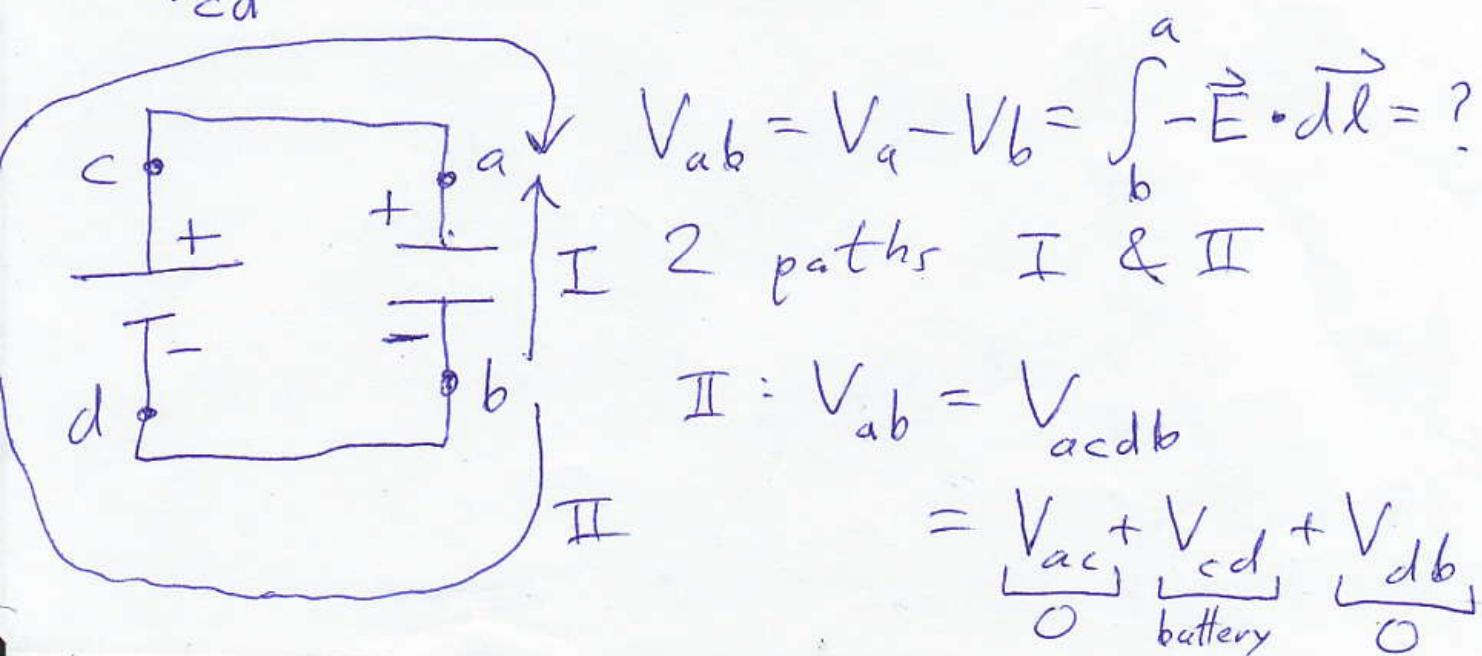
$$V_{cd} = \text{voltage of battery} = \text{constant}$$




$$V_{ab} = V_{cd}$$

Key idea:

"conservativity of electrostatic field"
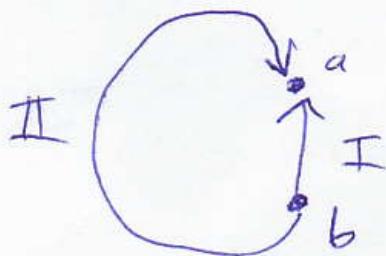
$$V_{ab} = \int_I -\vec{E} \cdot d\vec{l} = \int_{\#} -\vec{E} \cdot d\vec{l}$$



Other key idea: conservation of (net) charge

Suppose we change a capacitor with a battery. We can

insert a dielectric, say, paper,

- (1) with the battery connected, or
- (2) without the battery connected.

$$\frac{Q}{V} = C_0 = \frac{A\epsilon_0}{d} \text{ before paper} \quad C_0 = \frac{Q_0}{V_0}$$


$$\frac{Q}{V} = C = \frac{AKe_0}{d} \text{ after paper (K=3.7)}$$

V_0 = battery voltage


Case (1) : $V = V_0$, so

$$\frac{Q}{V} = \frac{Q_0}{V_0} = C = K C_0 = \frac{K Q_0}{V_0} \Rightarrow Q = K Q_0$$
$$\Rightarrow U = K U_0$$

Case (2) :

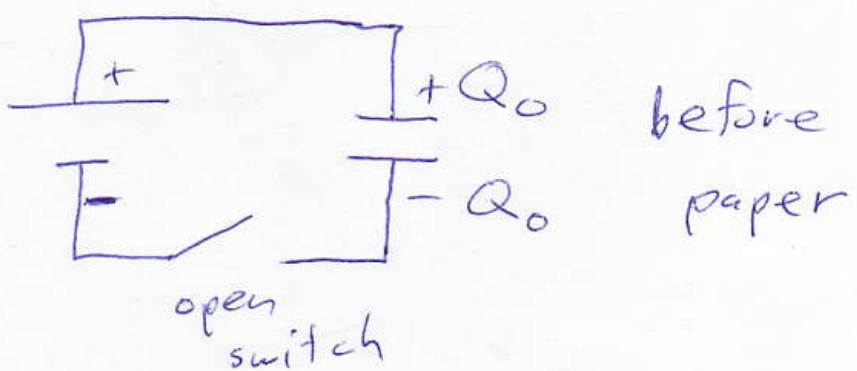

conservation
of charge

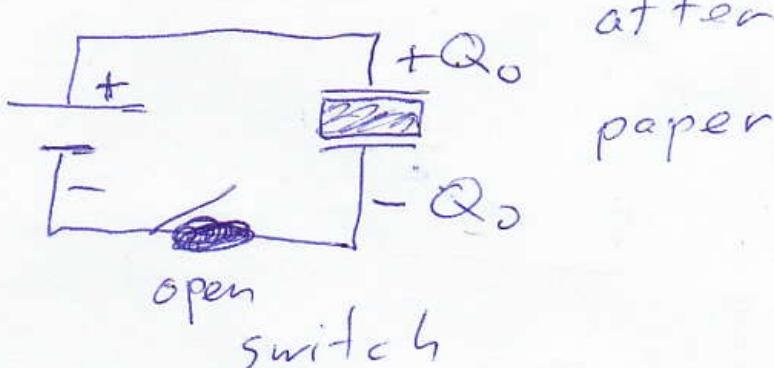


$$Q = Q_0$$

$$\frac{Q}{V} = \frac{Q_0}{V} = C = K C_0 = \frac{K Q_0}{V_0} \Rightarrow V = \frac{V_0}{K}$$
$$\Rightarrow U = U_0 / K$$

$$U = \frac{Q^2}{2C} \xrightarrow[C = Q/V]{Q/V} = \frac{CV^2}{2}$$

↑ energy to charge capacitor from 0 to Q

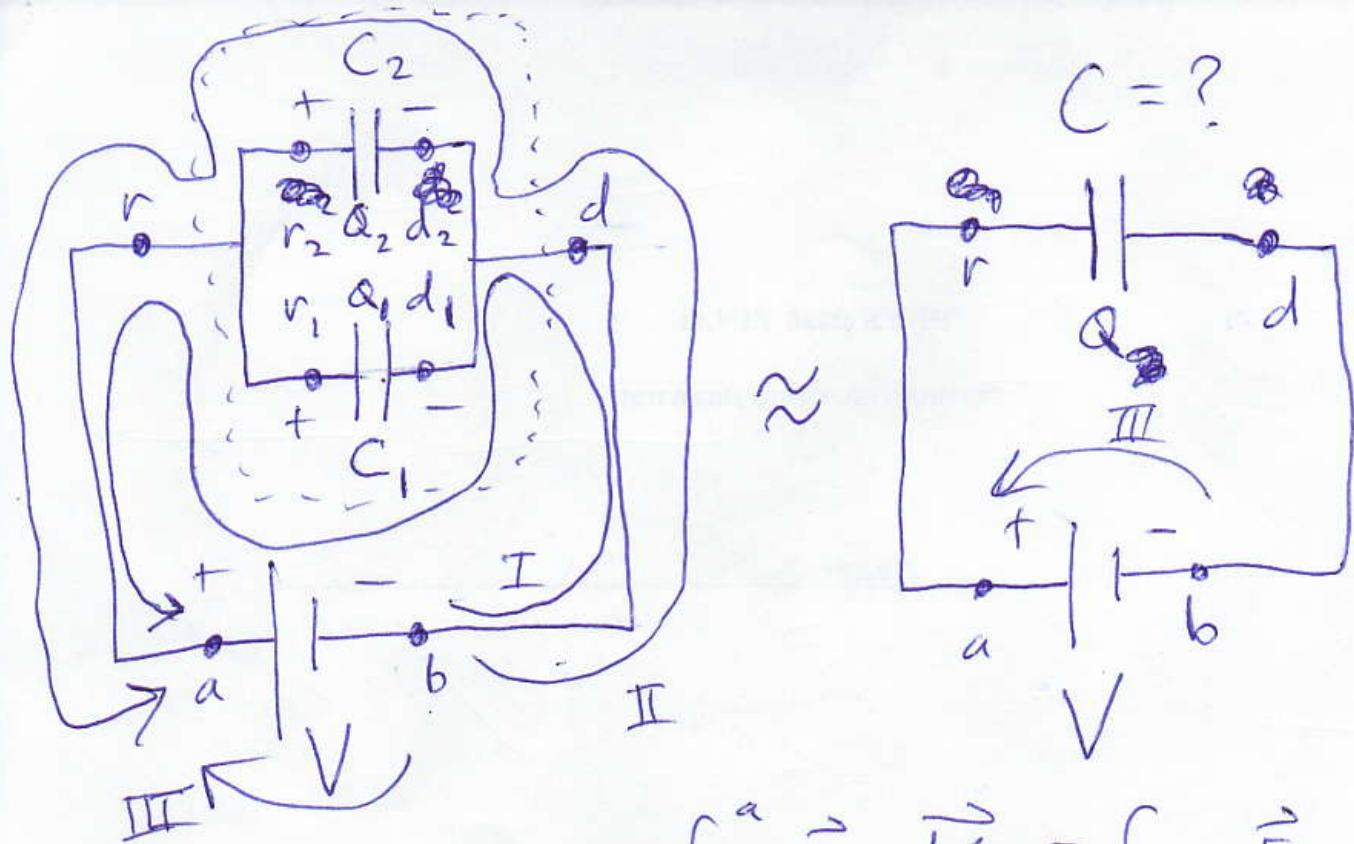


$$V = V_{ab} = V_a - V_b = \int_b^a -\vec{E} \cdot d\vec{l} = \int_{III} -\vec{E} \cdot d\vec{l}$$

$$V = V_{ab} = \underbrace{\int_I -\vec{E} \cdot d\vec{l}}_{V_{r_1 d_1}} = \underbrace{\int_{II} -\vec{E} \cdot d\vec{l}}_{V_{r_2 d_2}} = V_{rd}$$

$$Q = Q_1 + Q_2$$

$$V = V_{rd} = V_{r_1 d_1} = V_{r_2 d_2}$$
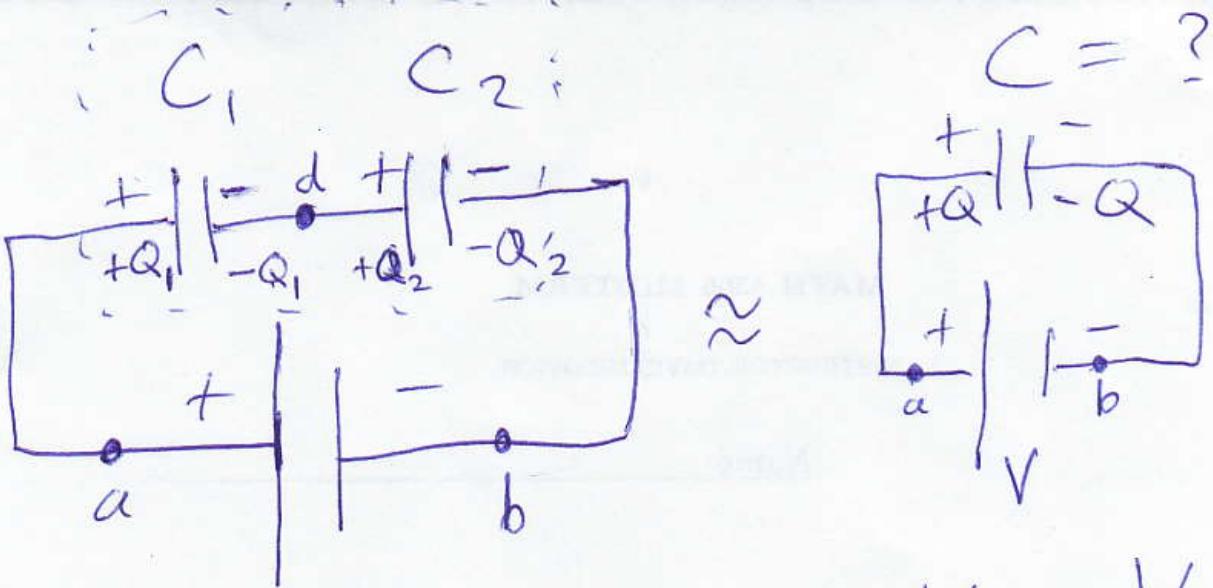
$$C = \frac{Q}{V} = \frac{Q_1 + Q_2}{V} = \frac{Q_1}{V} + \frac{Q_2}{V} = C_1 + C_2$$



$$V_{ab} = V_{adb} = \frac{V_{ad}}{C_1} + \frac{V_{db}}{C_2}$$

$\frac{d}{\text{net charge } 0}$
is conserved

$$0 = -Q_1 + Q_2 \Rightarrow Q_1 = Q_2 = Q$$

E.g. $C_1 = 470 \mu F$
 $C_2 = 300 \mu F$

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{C_2 + C_1}{C_1 C_2}$$

$$C = \frac{C_1 C_2}{C_1 + C_2} = 183 \mu F$$