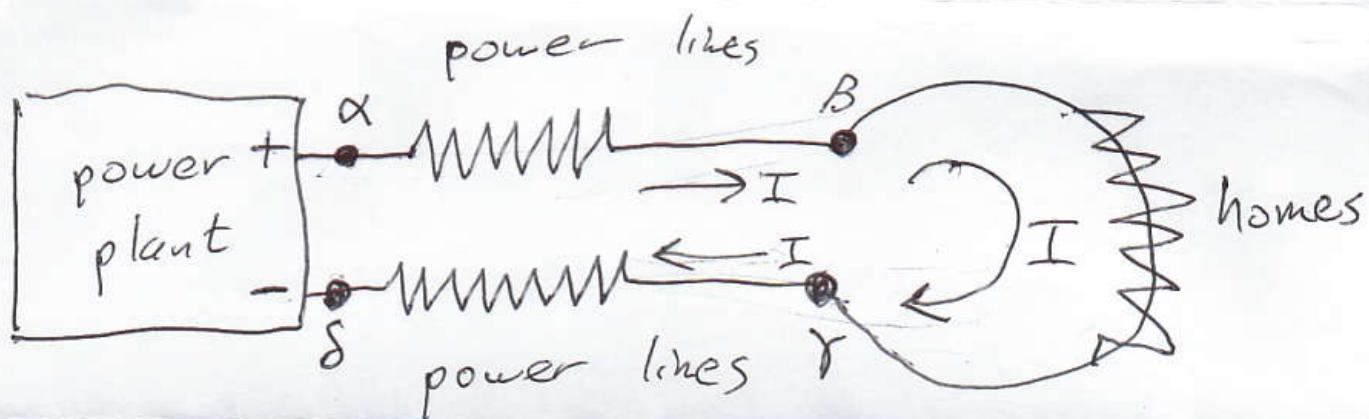


Power transmission:

1.0×10^5 homes, 2.0×10^3 W per home



transmission loss: $P_{\alpha\beta} + P_{\gamma\delta}$ 2.0×10^2 MW

useful electrical power: $P_{\beta\gamma} = 2.0 \times 10^8$ W

total power generated: $P_{\alpha\beta} + P_{\gamma\delta} + P_{\beta\gamma}$

$$e = \text{efficiency} = \frac{P_{\beta\gamma}}{P_{\alpha\beta} + P_{\beta\gamma} + P_{\gamma\delta}} \leftarrow 200 \text{ MW}$$

What should $V_{\alpha\beta}$ be to get $e = \underbrace{0.99}_{99\%}$?

power lines: aluminum: $\rho = 2.8 \times 10^{-8} \Omega \cdot \text{m}$

$$l = 1.0 \times 10^2 \text{ km} = 1.0 \times 10^5 \text{ m} \quad R = \frac{\rho l}{A}$$

$$d = 30 \text{ cm}$$

$$A = \pi r^2 = \pi \left(\frac{d}{2}\right)^2$$

$$A = 7.069 \times 10^{-4} \text{ m}^2$$

$$d = 3.0 \times 10^{-2} \text{ m}$$

$$V = IR$$

$$V_{\alpha\delta} = V_{\alpha\beta\gamma\delta} = V_{\alpha\beta} + V_{\beta\gamma} + V_{\gamma\delta}$$

$$P = IV$$

$$P_{\alpha\beta} = I \cancel{V_{\alpha\beta\gamma\delta}} V_{\alpha\beta} = IIR_{\text{line}}$$

$$200 \text{ MW} = P_{\text{homes}} = P_{\beta\gamma} = IV_{\beta\gamma} = IIR_{\text{homes}}$$

$$P_{\gamma\delta} = IV_{\gamma\delta} = IIR_{\text{line}}$$

$$0.99 = e = \frac{P_{\text{homes}}}{P_{\text{homes}} + 2I^2R_{\text{line}}}$$

$$R_{\text{line}} = \frac{\rho l}{A} = \frac{(2.8 \cdot 10^{-8} \Omega \cdot \text{m}) \cdot (10 \times 10^5 \text{ m})}{7.069 \cdot 10^{-4} \text{ m}^2}$$

$$R_{\text{line}} = 3.961 \Omega$$

$$\frac{1}{e} = \frac{P_{\text{homes}} + 2I^2R_{\text{line}}}{P_{\text{homes}}}$$

$$\frac{P_{\text{homes}}}{e} = P_{\text{homes}} + 2I^2R_{\text{line}}$$

$$P_h \left(\frac{1}{e} - 1 \right) = \frac{P_{\text{homes}}}{e} - P_{\text{homes}} = 2I^2R_{\text{line}}$$

$$\frac{P_h \left(\frac{1}{e} - 1\right)}{2R} = I^2 \Rightarrow \sqrt{\frac{P_h \left(\frac{1}{e} - 1\right)}{2R}} = I$$

$$I = \sqrt{\frac{W}{\Omega}} 5.0497 \times 10^2 = 5.0 \times 10^2 A$$

$$\Omega = V/A = \frac{\frac{J}{C}}{\frac{C}{s}} = \frac{J}{C} \cdot \frac{s}{C} = \frac{J \cdot s}{C^2}$$

$$W = J/s$$

$$\frac{W}{\Omega} = \frac{\frac{J}{s}}{\frac{J \cdot s}{C^2}} = \cancel{\frac{J}{s}} \frac{C^2}{\cancel{J \cdot s}} = \frac{C^2}{s^2} = A^2$$

$$5.0 \times 10^2 A$$

$$4.0 \Omega$$

$$P_{\alpha\beta} + P_{\gamma\delta} = I^2 R_{line} + I^2 R_{line} = 2 I^2 R_{line}$$

transmission loss

$$2.02 \times 10^6 W$$

$$A^2 \Omega = W$$

$$2.0 \times 10^8 W = P_{homes} = P_{\beta\gamma} \quad \cancel{P_{\alpha\beta}}$$

$$\text{total power} = P_{\alpha\beta} + P_{\beta\gamma} + P_{\gamma\delta} = I \underbrace{(V_{\alpha\beta} + V_{\beta\gamma} + V_{\gamma\delta})}_{V_{\alpha\delta}}$$

$$V_{\alpha s} = \frac{2.0 \times 10^8 W + 2.02 \dots \times 10^6 W}{I} \rightarrow 5.0 \times 10^2 A$$


$$V_{\alpha s} = 4.0 \times 10^5 V$$

high voltage for efficient transmission
lower voltage for safety

What should the voltage $V_{\alpha s}$ be
for 99.99% efficiency?

Kirchoff's laws (Ch. 26)

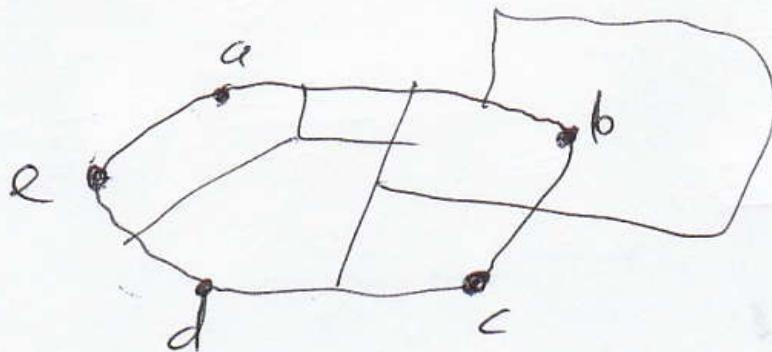
Loop law: In a loop of a circuit,
the ~~voltage~~ drop along the loop is 0.



$$0 = V_{abcdea} = V_{ab} + V_{bc} + V_{cd} + V_{de} + V_{ea}$$

$$\text{Equiv: } -V_{ea} = V_{ae} = V_{ab} + V_{bc} + V_{cd} + V_{de}$$


Junction law:

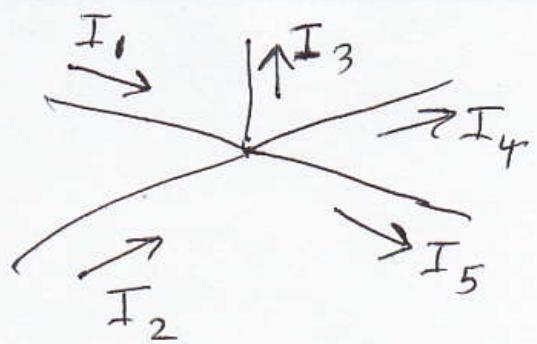

At junctions, current in = current out

$$I_1 + I_2 = I_3 + I_4 + I_5$$

(I's can be + or -.)

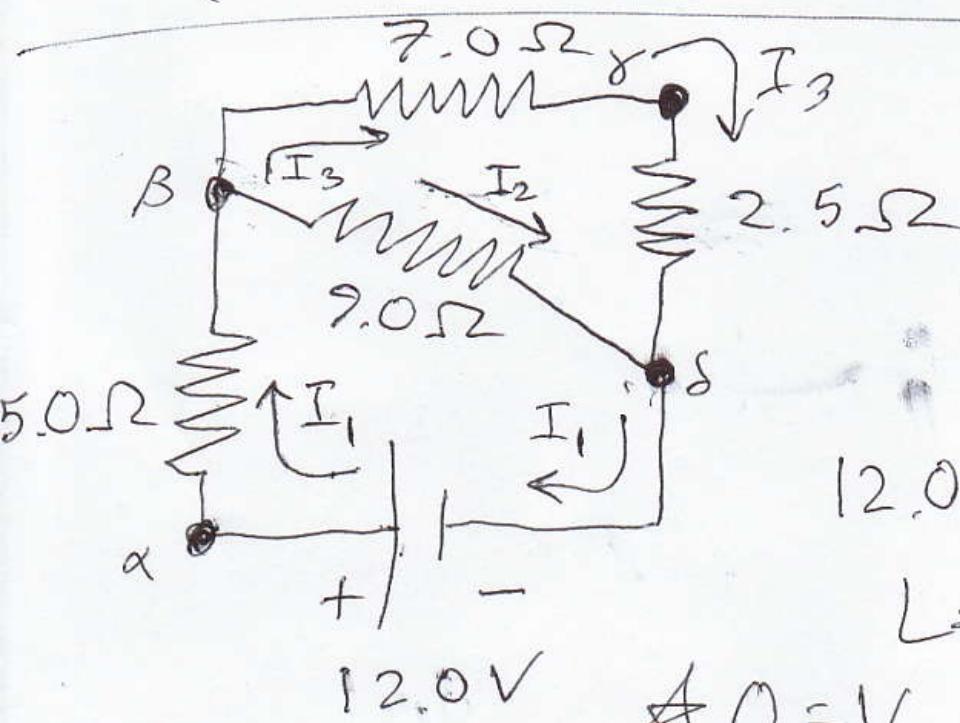

Junction law


$$\text{at } \beta: I_1 = I_2 + I_3$$

$$\text{at } \delta: I_2 + I_3 = I_1$$

$$12.0V = V_{\alpha} - V_{\delta} = V_{\alpha\delta}$$

Loop law:
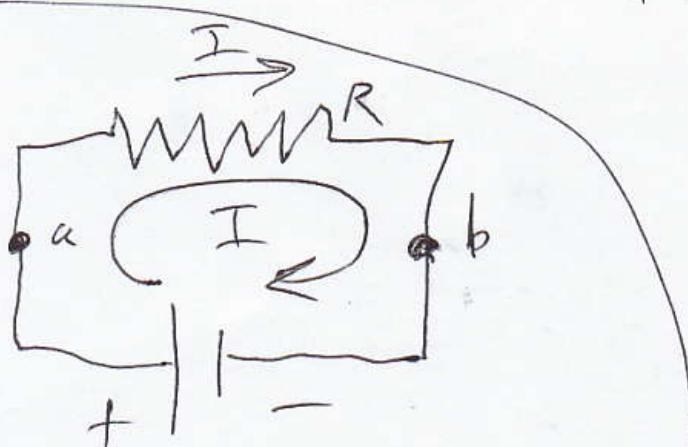
$$\text{at } O: 0 = V_{\alpha\beta\delta\alpha} = \underbrace{V_{\alpha\beta}}_{I_1(5.0\Omega)} + \underbrace{V_{\beta\delta}}_{-12.0V} + \underbrace{V_{\delta\alpha}}_{I_2(9.0\Omega)}$$



$$-V_{ba} = V_{ab} = IR$$

$$0 = V_{\beta\gamma\delta\beta} = V_{\beta\gamma} + V_{\gamma\delta} + V_{\delta\beta}$$

$$\cancel{0 = I_3(7.0\Omega) + (2.5\Omega)I_3 - I_2(9.0\Omega)}$$

Solve the 3 ~~*~~'s for I_1 , I_2 , I_3 .

To find voltages, use $V = (\pm) IR$:

$$V_A - V_B = V_{AB} = (5.0\Omega) I_1 \quad V_{BS} = (9.0\Omega) I_2$$
$$V_B - V_S = V_{BS} = (7.0\Omega) I_3 \quad V_B - V_S$$

$$I_1 = I_2 + I_3$$

$$= I_1(5.0\Omega) + I_2(9.0\Omega) - 12.0V$$

$$= I_3(7.0\Omega) + I_3(2.5\Omega) - I_2(9.0\Omega)$$

$$\frac{12.0V}{\Omega} = \frac{I_1(5.0\Omega) + I_2(9.0\Omega)}{\Omega}$$

$$12.0A = 5.0I_1 + 9.0I_2$$

$$0 = 9.5I_3 - 9.0I_2$$

$$12.0A = 5.0(I_2 + I_3) + 9.0I_2$$

$$12.0A = 14.0I_2 + 5.0I_3$$

$$\begin{cases} 0 = -9.0I_2 + 9.5I_3 & (\text{eq}_1) \\ 12.0A = 14.0I_2 + 5.0I_3 & (\text{eq}_2) \end{cases}$$

$$14\text{eq}_1 + 9\text{eq}_2 : 108A = 0 + 178I_3$$

$$0.61A = \frac{108A}{178} = I_3$$

$$5\text{eq}_1 - 9.5\text{eq}_2 : -114A = -178I_2 + 0$$

$$0.64A = \frac{-114A}{-178} = I_2$$

$$I_1 = I_2 + I_3 = 1.25A$$

Then find $V_{\alpha\beta}$, $V_{\beta\gamma}$, $V_{\gamma\delta}$...

$$V_{\alpha\beta} = I_1(5.0\Omega) = 6.3V$$

Bonus:

$$P_{\alpha\beta} = I_1^2(5.0\Omega) = 7.8W$$

$$V_{\beta\gamma} = I_3(7.0\Omega) = 4.2V$$

$$P_{\beta\gamma} = I_3^2(7.0\Omega) = 2.6W$$

$$V_{\gamma\delta} = I_3(2.5\Omega) = 1.5V$$

$$P_{\gamma\delta} = I_3^2(2.5\Omega) = 0.92W$$

$$V_{\beta\delta} = I_3(9.0\Omega) = 5.8V$$

$$P_{\beta\delta} = I_3^2(9.0\Omega) = 3.7W$$

total power: $P_{\alpha\beta} + P_{\beta\gamma} + P_{\gamma\delta} + P_{\beta\delta}$

equals 15.0W, which equals
 $I_1 \cdot V_{\alpha\delta} = (1.25A)(12.0V)$.

$$P = IV = I^2R$$

$$(also, P = IV = V^2/R)$$