

Close the switch.

Then, After time $\tau = RC$,

$$Q = e^{-t} Q_0 \text{ on capacitor}$$

$$e^{-1} = 0.3678794\dots$$

Here's why: $q(t) = \text{charge}$

on positive plate @ time t after
switch closed. $dq/dt = -I$

$$C = \frac{q}{V} \quad R = \frac{V}{I} \quad C, R \text{ constant}$$

$$I = \frac{V}{R} = \frac{q/C}{R} = \frac{q}{RC} \Rightarrow \frac{dq}{dt} = -\frac{q}{RC}$$

$$\Rightarrow \frac{dq}{q} = -\frac{1}{RC} dt \Rightarrow \int_{Q_0}^Q \frac{dq}{q} = -\frac{1}{RC} \int_0^t dt$$


$$\int_{3m}^{5m} \frac{dx}{x} = \underbrace{\ln(5m) - \ln(3m)}_{\text{nonsense}}$$

$$\ln \frac{Q}{Q_0} = \frac{-t}{\tau}$$

$$= \ln \frac{5m}{3m} = \ln \frac{5}{3} \quad \frac{Q}{Q_0} = e^{-t/\tau} \quad \tau = RC$$

$$q = Q = Q_0 e^{-t/\tau}$$
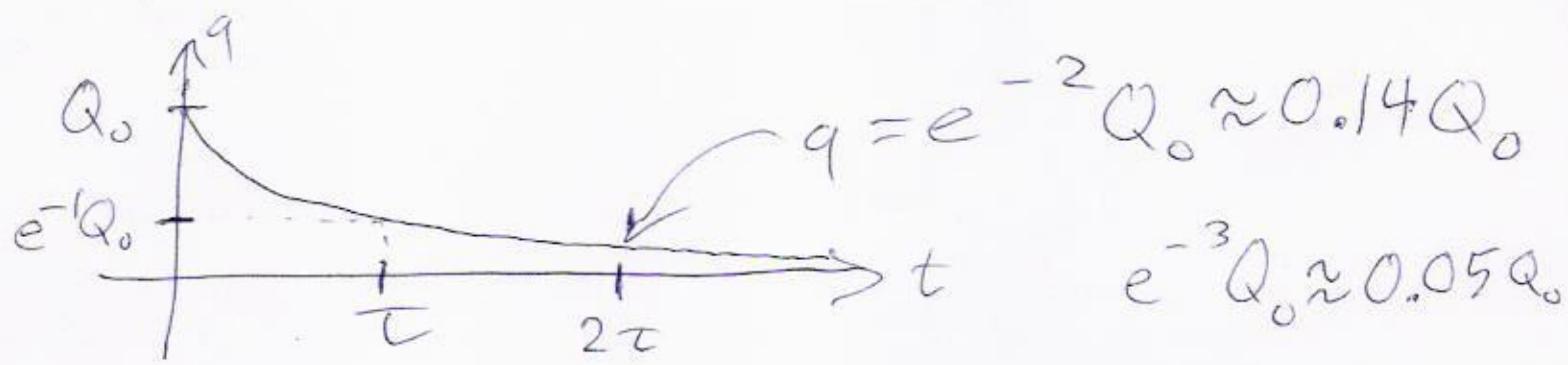
$$t = \tau \Rightarrow Q = Q_0 e^{-\tau/\tau} = Q_0 e^{-1}$$



$$I = - \cancel{\frac{dq}{dt}} = -Q_0 \left(-\frac{1}{\tau}\right) e^{-t/\tau}$$

$$\boxed{I = \frac{Q_0}{\tau} e^{-t/\tau} \quad t=0 \Rightarrow I_0 = \frac{Q_0}{\tau} e^0 = \frac{Q_0}{\tau}}$$

$$\boxed{V = \frac{Q}{C} = \frac{Q_0}{C} e^{-t/\tau} \quad t=0 \Rightarrow V_0 = \frac{Q_0}{C} e^0 = \frac{Q_0}{C}}$$

$$U = \text{energy in capacitor} = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} C V^2 = \frac{1}{2} Q V = \boxed{\frac{Q_0}{2C} e^{-\frac{2t}{\tau}}}$$

$\rightarrow P = IV = \cancel{\text{rate}} \text{ at which resistor converts current into heat}$

$$\boxed{P = \frac{Q^2}{\tau C} e^{-2t/\tau} = P_0 e^{-2t/\tau}}$$

$$t = \tau \Rightarrow P = P_0 e^{-2} \approx 0.14 P_0$$


$$\rightarrow \frac{dU}{dt} = -P \Rightarrow U = \boxed{\int_0^t -P dt} = \boxed{\frac{P_0 \tau}{2} e^{-\frac{2t}{\tau}}}$$

$$e^{-10} = 4.5 \dots \times 10^{-5}$$

Waiting 10 τ
is as good
as waiting forever.

Charging a capacitor

$t=0: q=0$ (switch closed)

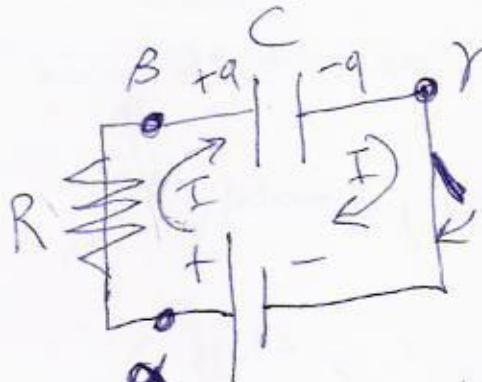

Time t after switch closed: $q = ?$

$$V_0 = \text{constant} \quad V_{\alpha\gamma} = V_0 = \text{const}$$

$$V_0 = V_{\alpha\gamma} = V_{\alpha\beta\gamma} = \underbrace{V_{\alpha\beta}}_{IR} + \underbrace{V_{\beta\gamma}}_{q/C}$$

$$\frac{dq}{dt} = I \Rightarrow V_0 = \frac{dq}{dt} R + \frac{q}{C}$$

$$V_0 - \frac{q}{C} = \frac{dq}{dt} R \Rightarrow dt(V_0 - q/C) = R dq$$

$$\int_0^t \frac{dt}{\tau} = \int_0^q \frac{dq}{Q_{\max} - q} \quad \boxed{\circlearrowleft} \quad dt = \frac{R dq}{V_0 - q/C}$$

$$u = Q_{\max} - q$$

$$du = -dq$$



$$\tau \rightarrow \frac{RC}{(CV_0) - q} dq$$

$$t = \int_{Q_{\max}-0}^{Q_{\max}-q} \frac{-du}{u} = \int_{Q_{\max}-q}^{Q_{\max}-0} \frac{dy}{u}$$

$$\frac{t}{\tau} = \ln \frac{Q_{\max}}{Q_{\max}-q} \Rightarrow e^{\frac{t}{\tau}} = \frac{Q_{\max}}{Q_{\max}-q}$$

$$Q_{\max} e^{-t/\tau} = Q_{\max}-q \leftarrow e^{-t/\tau} = \frac{Q_{\max}-q}{Q_{\max}}$$
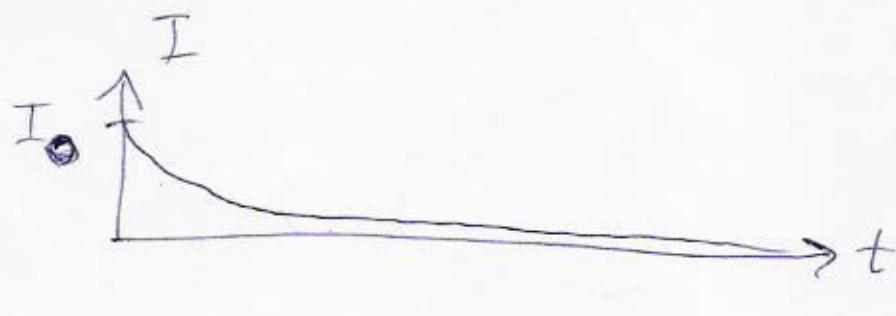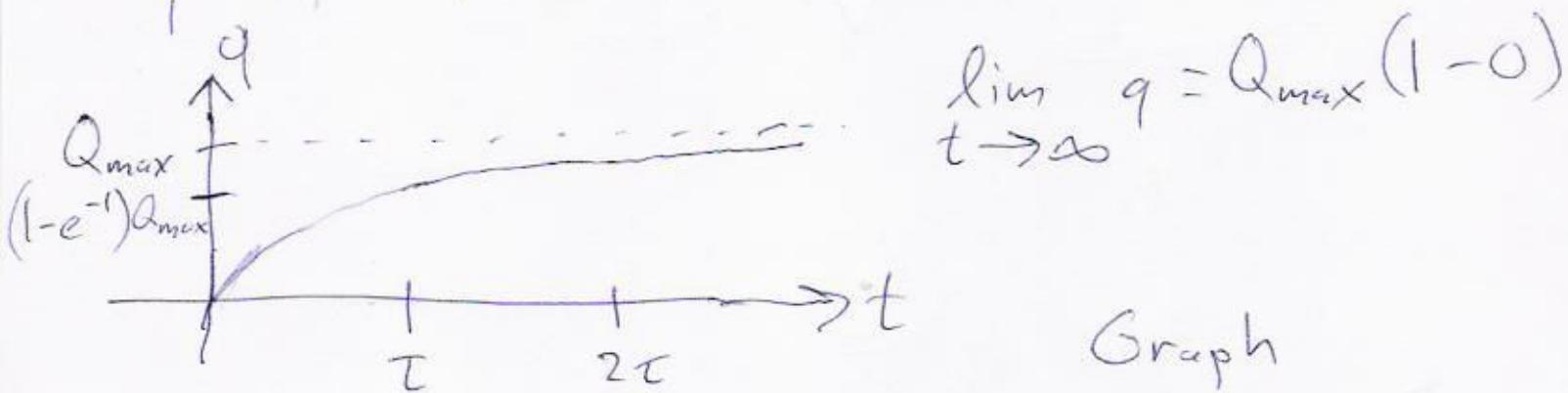
$$q = Q_{\max} - Q_{\max} e^{-t/\tau} = Q_{\max} (1 - e^{-t/\tau})$$




E.g. $R = 41 \Omega$ $C = 470 \mu F = 4.70 \times 10^{-4} F$



$$\tau = RC = (41 \cdot 4.7 \times 10^{-4}) s = 1.9 \times 10^{-2} s$$

$V_{\alpha\beta}, V_{B\gamma}$
 $P_{\alpha\beta}, U_{B\gamma}$,
 $P_{B\gamma}$, too...

Resistors in parallel & series


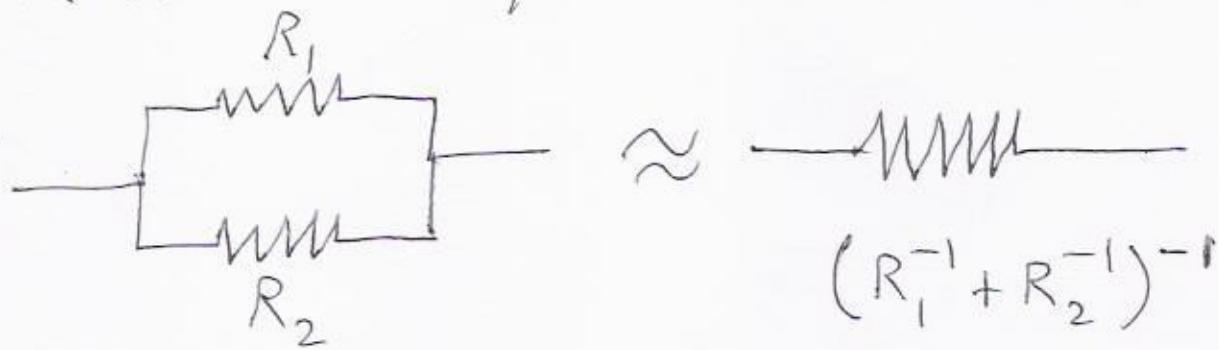


Compare to capacitors:-

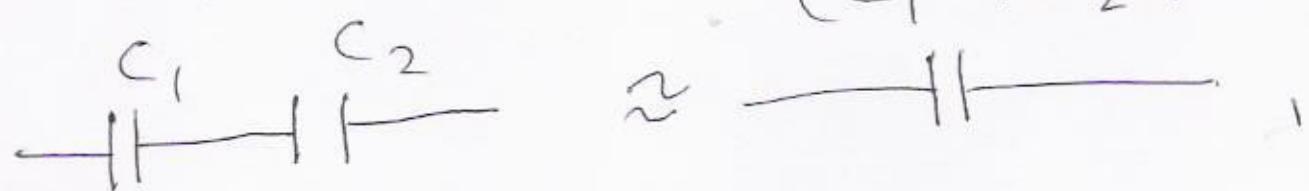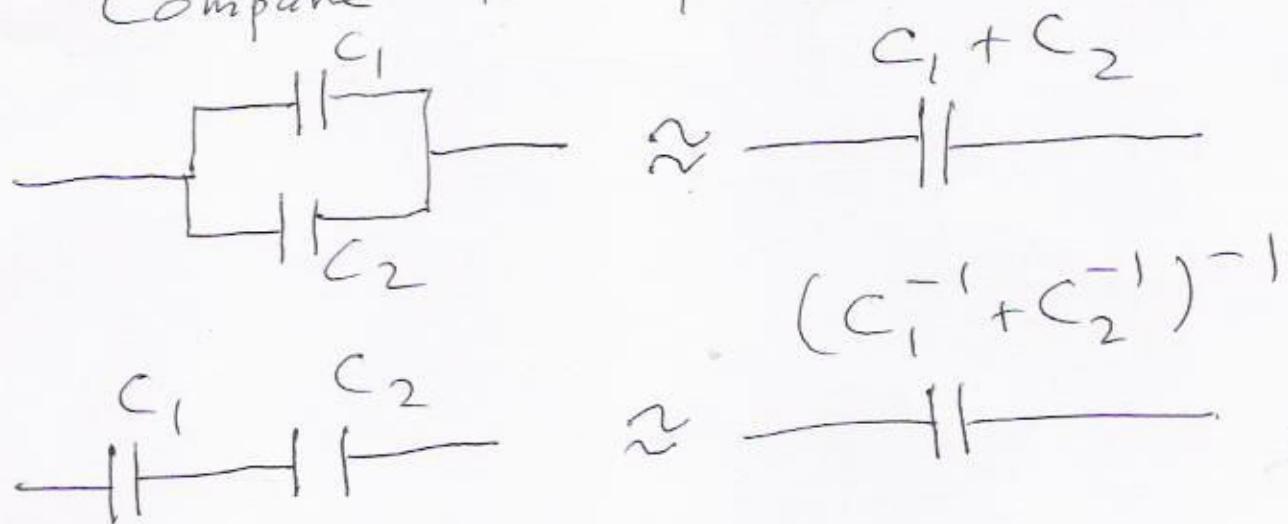


In more complicated circuits,
you may need to use Kirchoff's
rules (loop & junction) directly
to find R_{eq} & C_{eq} .

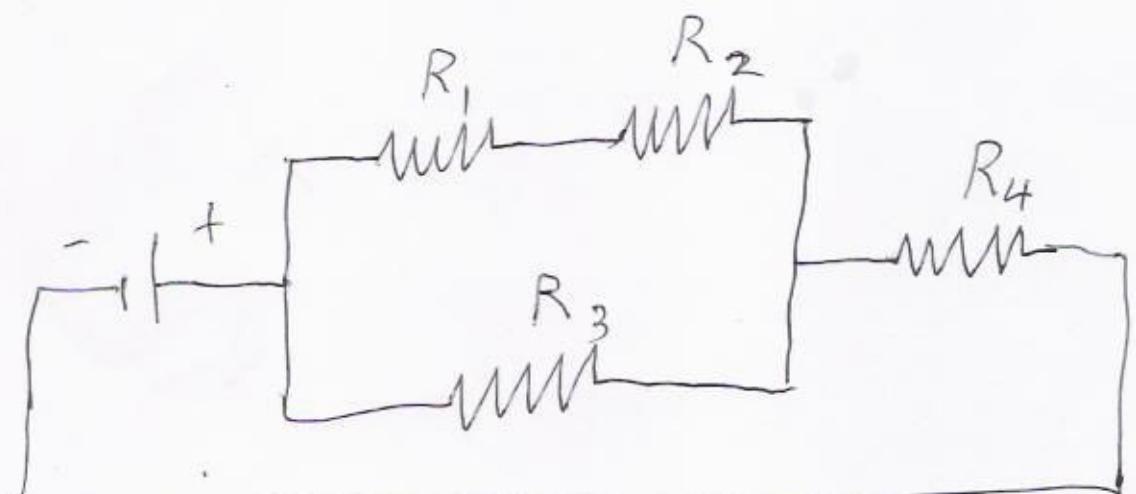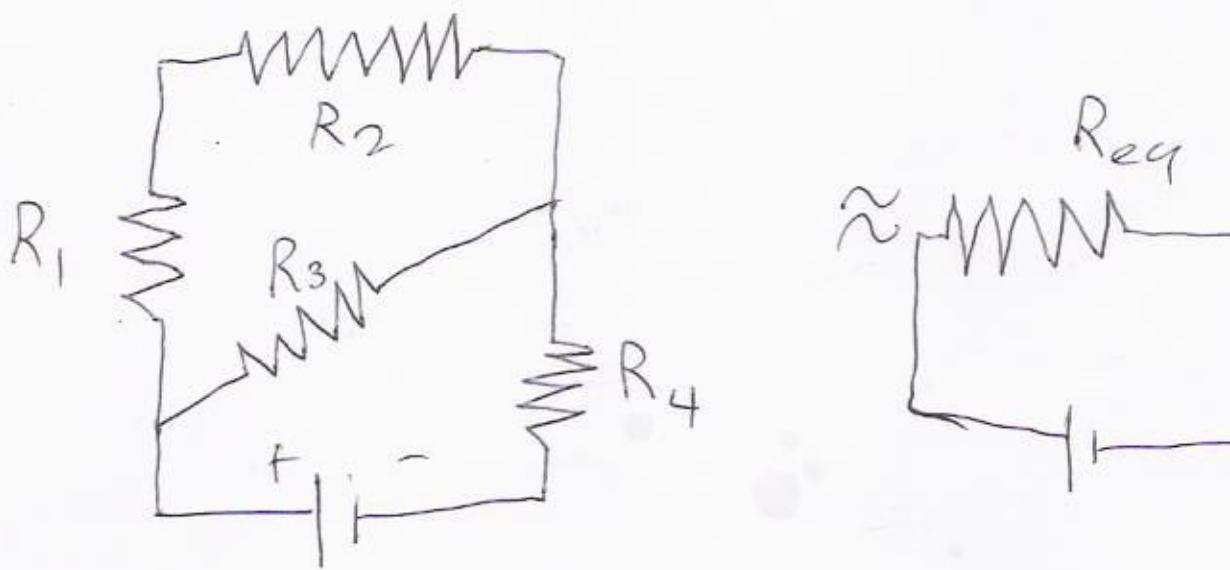Sometimes you can repeatedly use series
& parallel



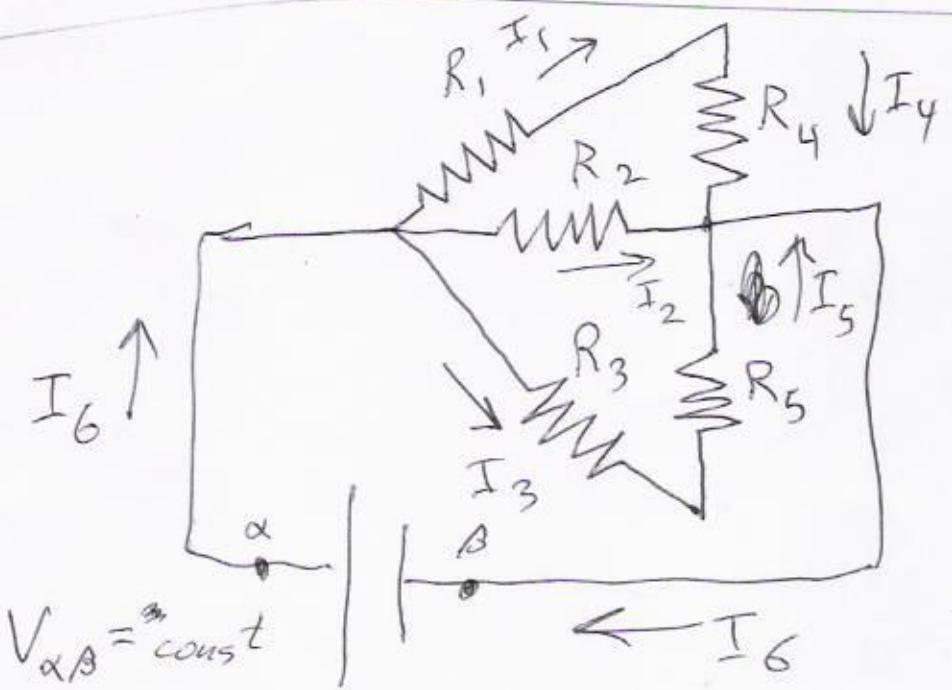
$$R_{eq} = ((R_1 + R_2)^{-1} + R_3^{-1})^{-1} + R_4$$



$$R_{eq} = ? = \frac{V_{\alpha\beta}}{I_6}$$

Takes more work...
Try Kirchhoff's rules


~~Actually, it's simpler:~~

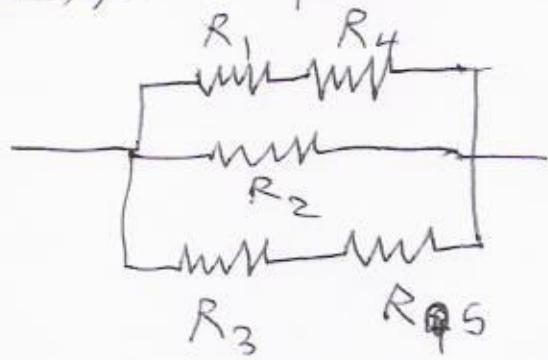

~~$\frac{1}{(R_1+R_4)} + \frac{1}{R_2} + \frac{1}{(R_3+R_5)}$~~

\approx
$$\frac{1}{\frac{1}{R_1+R_4} + \frac{1}{R_2} + \frac{1}{R_3+R_5}}$$

Here's a harder one:

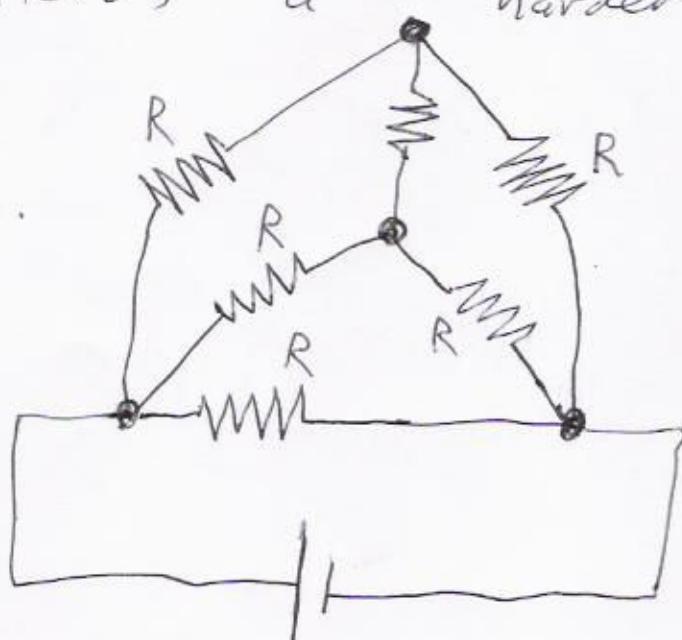

\approx
 $R_{eq} = ?$

Using Kirchhoff's Laws, I
computed $R_{eq} = \frac{1}{2} R$

Challenge problem:

Prove that

