








Appendix E:  
optional supplement  
to Ch. 31

Inductor

impedance for ac circuit	voltage response to current	stored energy	energy density	$P = VI$ power	$\tau$ time for $e^{-1}$ factor of decay of voltage & current
$Z = \omega L$ complex $Z = i\omega L$	 $V = L \frac{dI}{dt}$	$U = \frac{1}{2} L I^2$	$u = \frac{\mu}{2} B^2$ $\mu = K_m \mu_0$ $u = \frac{\mu_0}{2} B^2$ in absence of ferromagnetic stuff	$L I \frac{dI}{dt}$	$\tau = \frac{L}{R}$
<p>Capacitor</p> $Z = \frac{1}{\omega C}$ complex $Z = \frac{1}{i\omega C}$	 $V_{aB} = \frac{1}{C} \left( Q_0 + \int_0^t I dt \right)$	$U = \frac{1}{2} C V^2$	$u = \frac{1}{2} \frac{K \epsilon_0}{\epsilon} E^2$ $u = \frac{1}{2} \epsilon_0 E^2$ in absence of dielectric material	$C V \frac{dV}{dt}$	$\tau = RC$

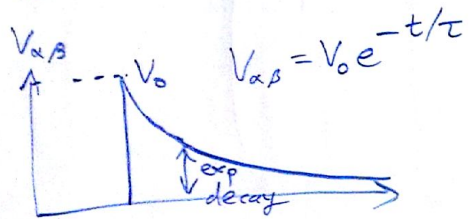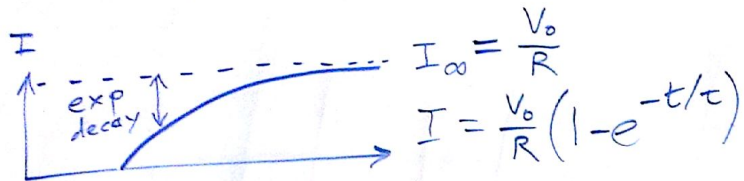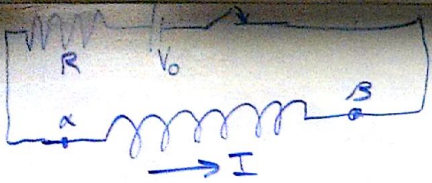

take away battery:

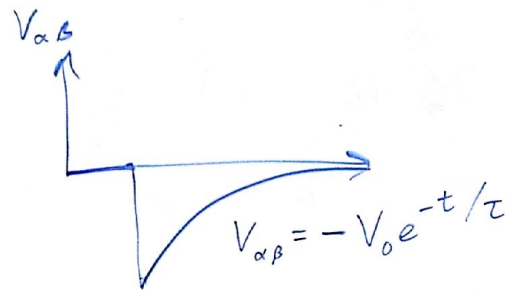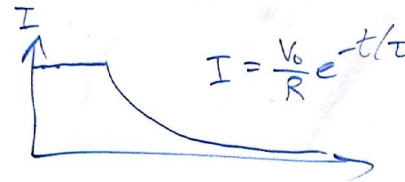

Fourier transform

$$f(t) = \frac{1}{\sqrt{2\pi}} \int_{-\infty}^{\infty} \hat{f}(\omega) e^{i\omega t} d\omega$$

$$\int f(t) dt = \frac{\hat{f}(\omega)}{i\omega}$$

$$\hat{f}'(t) = i \hat{f}(\omega) \omega$$