


The book uses the magnitude of impedance $|Z|$ and phase angle of impedance ϕ .

A better way is to have Z be a complex # that ~~also~~ encodes the magnitude & phase angle via $Z = |Z|e^{i\phi}$.

When using complex impedances:

impedances add in series



impedances' reciprocals add in parallel
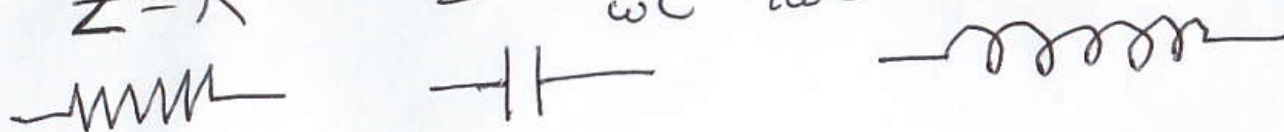
$$Z = R \quad Z = -\frac{i}{\omega C} = \frac{1}{i\omega C} \quad Z = i\omega L$$


The image shows three circuit symbols: a resistor (zigzag line), a capacitor (two parallel lines), and an inductor (coiled line).

Note: $\frac{1}{i} = -i$ because $i^2 = -1$


Example 1:

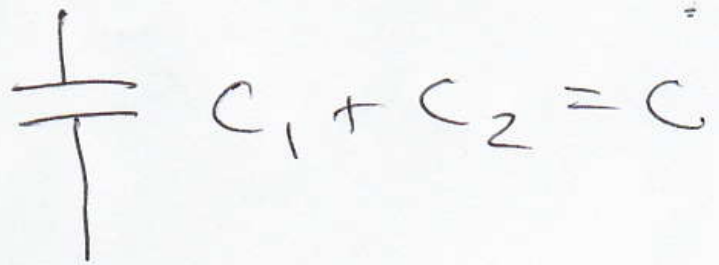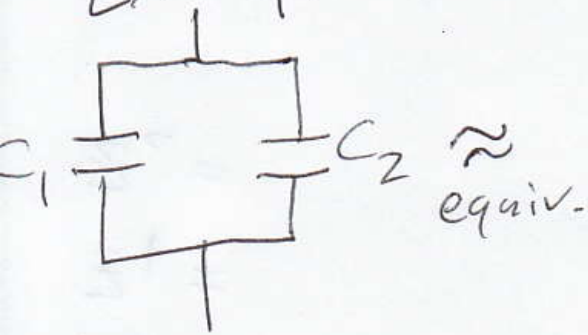

$$Z_1 = \frac{1}{i\omega C_1}, \quad Z_2 = \frac{1}{i\omega C_2} \Rightarrow Z = (Z_1^{-1} + Z_2^{-1})^{-1}$$

$$\Rightarrow Z = \frac{1}{Z_1^{-1} + Z_2^{-1}} = \frac{1}{i\omega C_1 + i\omega C_2} = \frac{1}{i\omega C} \quad \checkmark$$

Example 2:

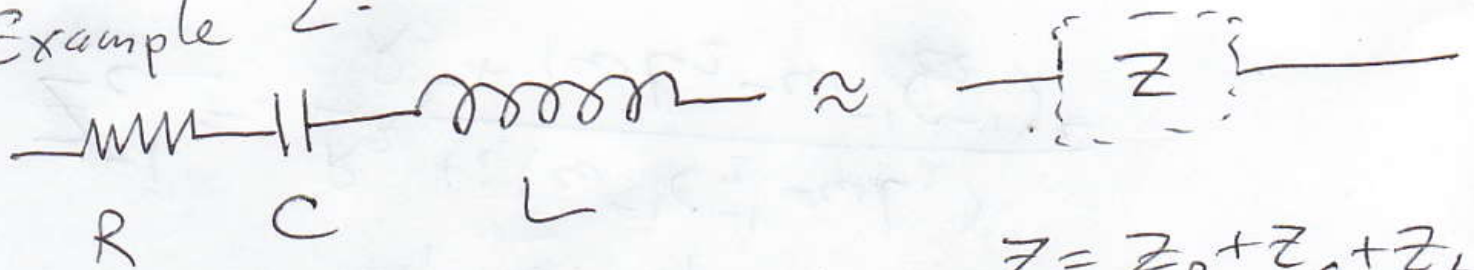

$$Z_R = R \quad Z_C = \frac{1}{i\omega C} \quad Z_L = i\omega L$$

$$Z = Z_R + Z_C + Z_L$$

$$Z = R + i\left(\frac{-1}{\omega C} + \omega L\right)$$

$$X_C = \frac{1}{\omega C} \quad \& \quad X_L = \omega L \Rightarrow Z = R + i(X_L - X_C)$$


● magnitude of impedance:

$$|a + bi| = \sqrt{a^2 + b^2}$$

$$|Z| = \sqrt{R^2 + (X_L - X_C)^2} \quad \text{just as in book}$$

phase angle ϕ of $a + bi = \arctan\left(\frac{b}{a}\right) \Rightarrow \phi = \arctan\left(\frac{X_L - X_C}{R}\right)$
 (for $a \geq 0$)

Example 3:

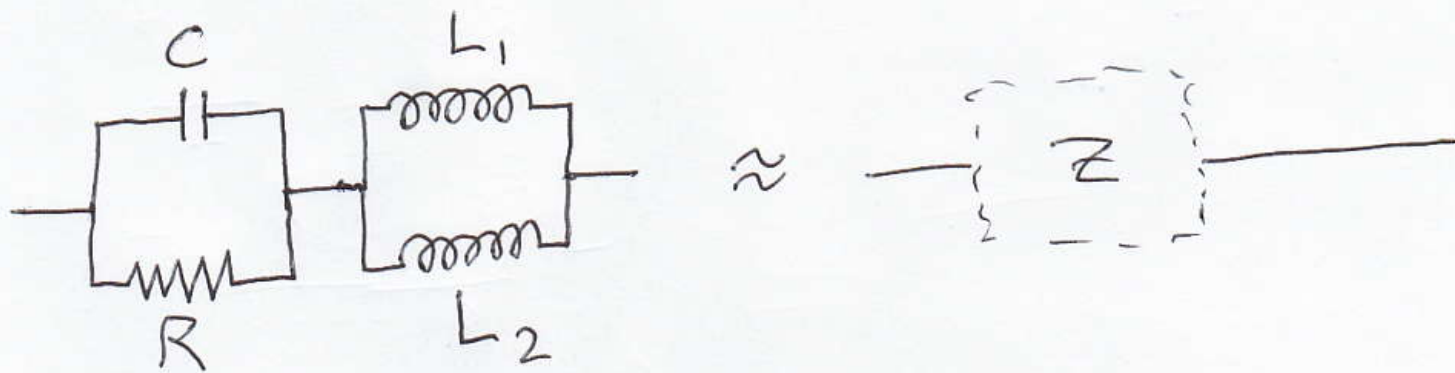

$$Z = (Z_R^{-1} + Z_C^{-1})^{-1} + (Z_{L_1}^{-1} + Z_{L_2}^{-1})^{-1}$$

$$Z = \left(\frac{1}{R} + i\omega C \right)^{-1} + \left(\frac{1}{i\omega L_1} + \frac{1}{i\omega L_2} \right)^{-1}$$

$$\textcircled{\text{a}} (a+bi)^{-1} = \frac{a-bi}{a^2+b^2} = \frac{a}{a^2+b^2} + i \frac{-b}{a^2+b^2}$$

$$Z = \frac{R^{-1} - i\omega C}{R^{-2} + \omega^2 C^2} + \frac{1}{i\omega} \left(\frac{1}{L_1} + \frac{1}{L_2} \right)^{-1}$$

$$Z = \frac{R^{-1}}{R^{-2} + \omega^2 C^2} - i \left[\frac{\omega C}{R^{-2} + \omega^2 C^2} + \frac{1}{\omega} \left(\frac{1}{L_1} + \frac{1}{L_2} \right)^{-1} \right]$$

$$|Z| = \sqrt{\left(\frac{R^{-1}}{R^{-2} + \omega^2 C^2} \right)^2 + \left(\frac{\omega C}{R^{-2} + \omega^2 C^2} + \frac{L_1 L_2}{\omega(L_1 + L_2)} \right)^2}$$

$$\left(\frac{1}{L_1} + \frac{1}{L_2} \right)^{-1} = \left(\frac{L_2 + L_1}{L_1 L_2} \right)^{-1} = \frac{L_1 L_2}{L_1 + L_2} \uparrow$$